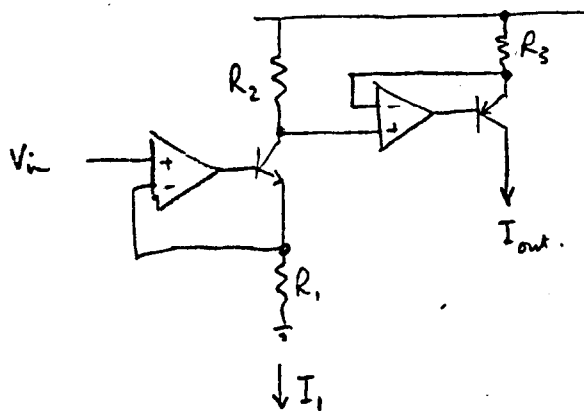


CH 4 SOLUTIONS  
OP AMPS

CHAPTER 4 PROBLEMS

3.1




$$I_1 = \frac{V_{in}}{R_1} \quad \text{since } + \text{ \& } - \text{ inputs are at same potential.}$$

$$\text{Voltage across } R_2 = V_{R_2} = I_1 R_2$$

$$I_{out} = \frac{V_{R_2}}{R_3} \quad (\text{as above})$$

$$I_{out} = \frac{I_1 R_2}{R_3} = \frac{V_{in} R_2}{R_1 R_3}$$

3.2

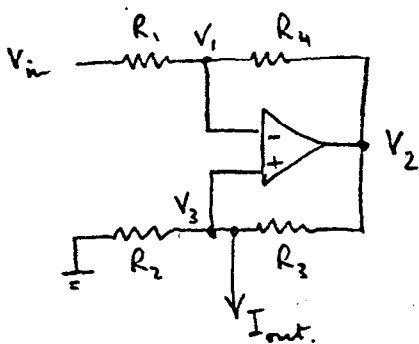


When op amp is balanced  $V_1 = V_3$

$$\frac{V_{in} - V_1}{R_1} = \frac{V_1 - V_2}{R_4}$$


$$I_{out} + \frac{V_1}{R_2} = \frac{V_2 - V_1}{R_3} = \left( \frac{V_1 - V_{in}}{R_3} \right) \frac{R_4}{R_1}$$

$$\frac{R_4}{R_3 R_1} = \frac{1}{R_2} \quad \text{by choice} \Rightarrow I_{out} + \frac{V_1}{R_2} = \left( \frac{V_1 - V_{in}}{R_2} \right) \Rightarrow I_{out} = -\frac{V_{in}}{R_2}$$

3.3 a)

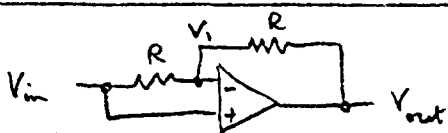

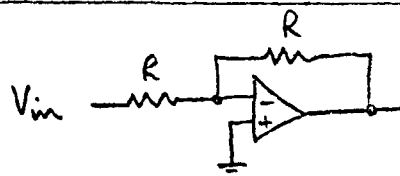
$$\left. \begin{aligned} V_1 &= V_{in} \text{ balance} \\ \frac{V_{in} - V_1}{R} &= \frac{V_1 - V_{out}}{R} \end{aligned} \right\} \Rightarrow V_{out} = V_{in}$$




$$\frac{V_{in}}{R} = -\frac{V_{out}}{R} \Rightarrow V_{out} = -V_{in}$$

b)

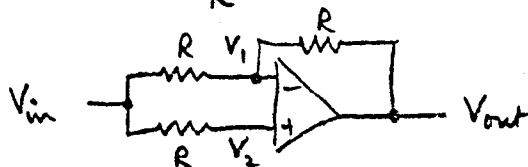


$$\left. \begin{aligned} V_1 &= V_2 \text{ balance} \\ V_{in} &= V_2 \text{ assuming no bias current} \end{aligned} \right\} \Rightarrow V_{out} = V_{in}$$
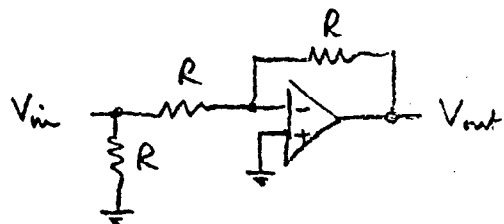
$$\frac{V_{in} - V_1}{R} = \frac{V_1 - V_{out}}{R}$$




As above:  $V_{out} = -V_{in}$

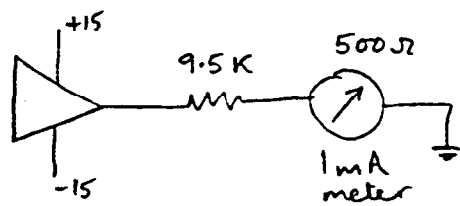3.4 Use the following trick to ensure that the maximum overload is  $< \pm 150\%$



Max output of opamp is  $\pm 13V$  (typical value).  
 $\Rightarrow$  max current is  $\frac{\pm 13V}{10K} = \pm 1.3mA$

Now construct the ammeter:

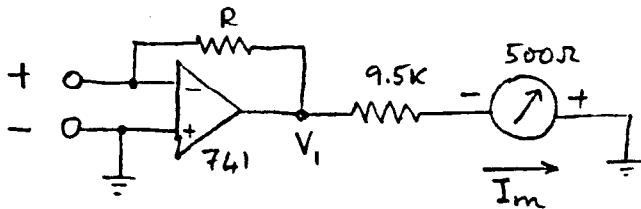


Voltage between inputs = 0 for perfect op amp.

Want to choose R so that  $I_m = -1mA$  when  $I_{in} = 5mA$

$$V_i = 10K \times I_m = -R I_{in}$$

$$R = -10K \frac{I_m}{I_{in}} = -10K \frac{-1}{5} = 2.0K\Omega$$

3.5

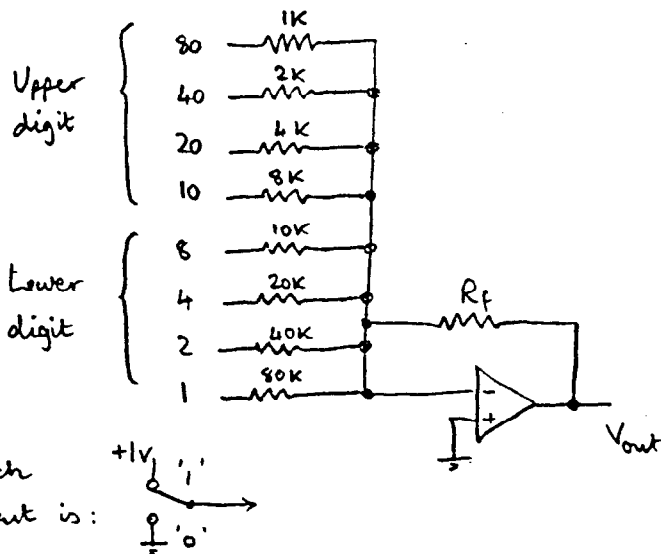

Choice of  $R_f$ :


Want  $V_{out} = -9.9V$  for digital input of '99'.

Thus 0.1V is the required increase in  $V_{out}$  per digit.

Voltage gain for '10' input is therefore -1.0

$$\Rightarrow R_f = 8K\Omega$$

3.6

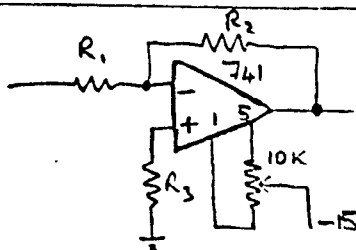


$$Z_{in} = R_1 = 10K \text{ by choice}$$

$$\text{Gain} = -\frac{R_2}{R_1} = -100 \Rightarrow R_2 = 1M\Omega$$


$$R_3 = R_1 \parallel R_2 = 10K$$

Add follower on input

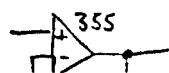

$$Z_{in} > 100M\Omega$$

3.7

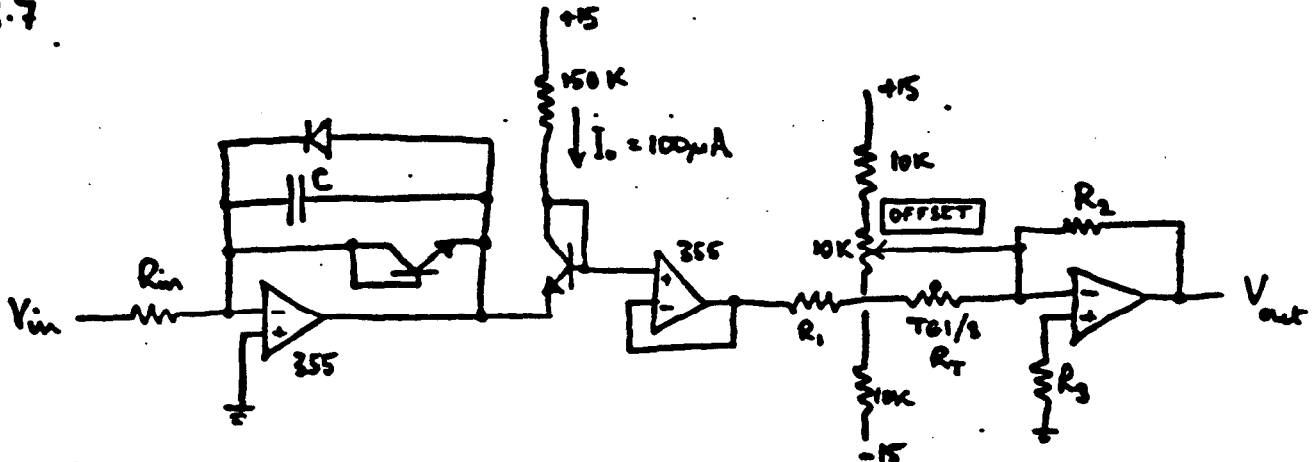

- a) A simple resistor to +15V is an adequate current source as the required compliance range is very small.
- b) Want combined resistance of  $R_T + R_1$  to have a tempo of  $\frac{1}{300} = 0.33\% \text{ degree}^{-1}$ . Then the gain will have the same tempo

$$\left. \begin{aligned} R &= R_1 + R_T \\ \frac{\Delta R}{\Delta T} &= \alpha R_T \end{aligned} \right\} \frac{1}{R} \frac{\Delta R}{\Delta T} = \frac{\alpha R_T}{R_1 + R_T} = 0.33\% \quad \begin{aligned} \alpha &= 0.7\% \\ R_T &= 2.7 \text{ K (300K)} \\ \Rightarrow R_1 &= 2.4 \text{ K} \end{aligned}$$

↑ temperature coefficient


$R = R_1 + R_T = 5.1 \text{ K}$  with the desired  $0.33\%$  tempo.

Want gain of final stage to be  $\frac{1 \text{ V decade}^{-1}}{-60 \text{ mV decade}^{-1}} = -16.7$


$\Rightarrow R_2 = 16.7 \times R = 82 \text{ K}$

$\Rightarrow R_3 = 82 \text{ K} \parallel 5.1 \text{ K} \parallel 15 \text{ K} \parallel 15 \text{ K} \approx 3 \text{ K} \Omega$ .


3.8

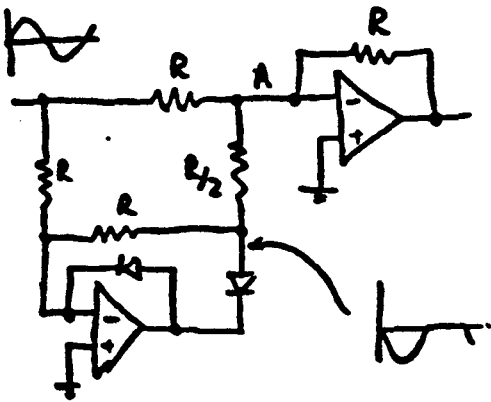


Summation of signals at A:

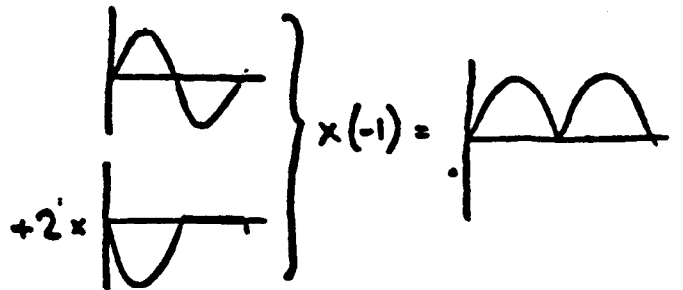


### 3.9 Schmitt Trigger:

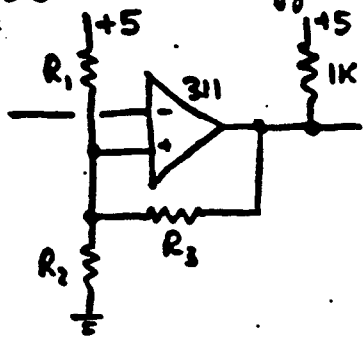

Lower threshold

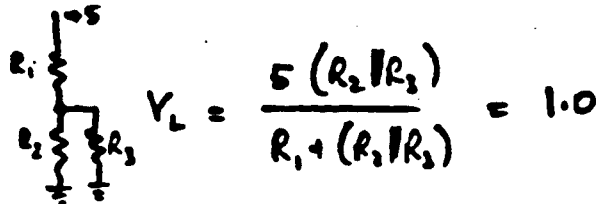

Upper threshold

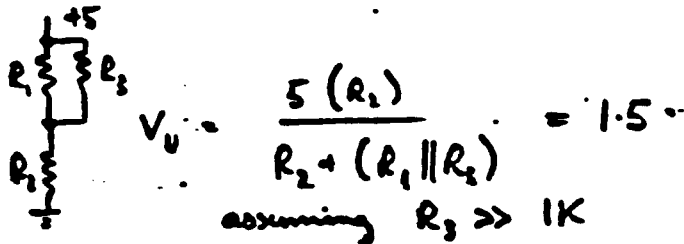

(It is always hard to avoid a lot of math with these problems!)

$$\frac{R_2 R_3}{R_2 + R_3} = 0.2 \left[ R_1 + \frac{R_2 R_3}{R_2 + R_3} \right] \Rightarrow 0.8 \frac{R_2 R_3}{R_2 + R_3} = 0.2 R_1 \quad \text{①}$$

$$R_2 = 0.3 \left[ R_2 + \frac{R_1 R_3}{R_1 + R_3} \right] \Rightarrow R_2 = \frac{1}{0.7} \left( \frac{R_1 R_3}{R_1 + R_3} \right) \Rightarrow \frac{1}{R_2} = 0.7 \left( \frac{1}{R_1} + \frac{1}{R_3} \right)$$

Substitute into ①:


$$4 = R_1 \left( \frac{1}{R_2} + \frac{1}{R_3} \right) = R_1 \left( 0.7 \left( \frac{1}{R_1} + \frac{1}{R_3} \right) + \frac{1}{R_3} \right) = 0.7 + 1.7 \frac{R_1}{R_3}$$

$$3.3 = 1.7 \frac{R_1}{R_3} \quad \text{Choose } R_3 = 22K \Rightarrow R_1 = 43K \Rightarrow R_2 = 20K$$


Math-saving trick (exam questions only!):

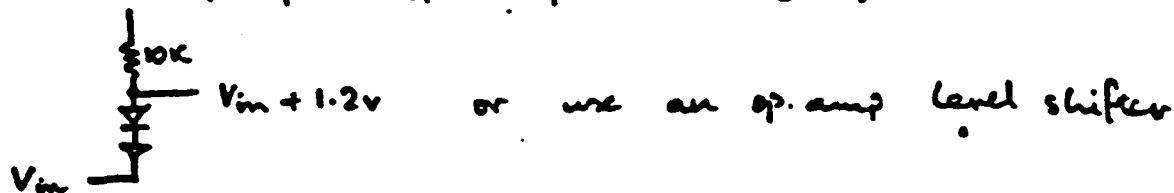i) shift level to centre of output swing

Here: midpoint of threshold = 1.25V  
midpoint of output = 2.5V } shift up 1.25V.



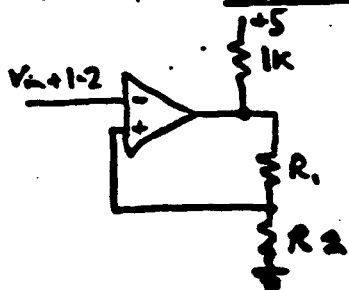ii) Use a symmetric Schmitt trigger. Here:



Want hysteresis = 0.5V

$$\Rightarrow \frac{R_2}{R_1 + R_2} = \frac{0.5V}{5V} \quad R_1 = 18K \quad R_2 = 2K$$

**3.10** Gain =  $(1 + \frac{27.8K}{R_i}) (-1)$

Scale	1st Stage $R_i$	2nd stage Gain	Variable gain set to max.
0 dB	$\infty$	-1	1
10	13.0K	-3.14	$\sqrt{10}$
20	3.09K	-10.0	10
30	909 $\Omega$	-31.6	$10\sqrt{10}$
40	280 $\Omega$	-100.3	100

- b) +5v reference  $\rightarrow$  potential divider  $\rightarrow$  0-5v variable  
 $\rightarrow$   $\times 2$  amplifier  $\rightarrow$  optional inverter ('offset pot')  
 $\pm 10v$  variable added with equal weight (equal  $R_{in}$ )  
 at summing (-) input of IC<sub>2</sub>.

3.12 Input presented at - pin of IC<sub>1</sub> is  $\frac{4.7}{4.7+4.7} V_{in} = 0.1 V_{in}$


DC voltage added to input at - pin is  $\frac{R_1}{R_4} = \frac{4.7K}{10M} \times 5 = 2.5mV$

Hysteresis =  $\begin{cases} \frac{4.7K}{4.7M} \times 5V = +5mV \text{ (upper)} \\ \frac{4.7K}{4.7M} \times 0V = 0 \text{ (lower)} \end{cases}$  when input is near zero

Thus thresholds are  $\pm 2.5mV$  to signals at the - pin  
 $\div (0.1) \rightarrow \pm 25mV$  to signals at the input.

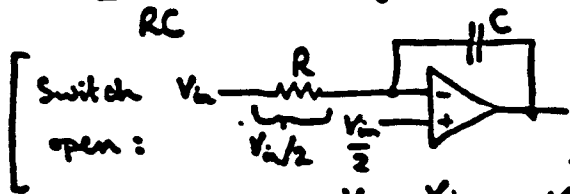
3.11 Rate of change of voltage at integrator output

=  $\pm \frac{V_{in}/2}{RC}$  volts s<sup>-1</sup>





Rate (open) =  $\frac{V_{in} - \frac{V_{in}}{3}}{RC} = \frac{V_{in}/2}{RC}$

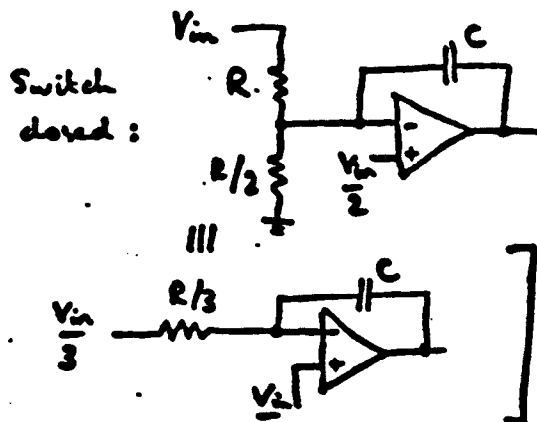Rate (closed) =  $\frac{(\frac{V_{in}}{3} - \frac{V_{in}}{2})}{\frac{R}{3}} = -\frac{V_{in}/2}{RC}$



(3.11 contd.)

Triangle out:

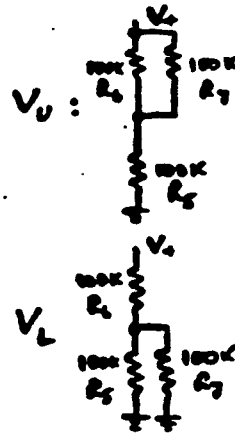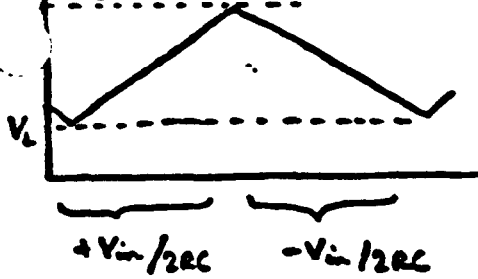

$$V_U = \frac{2}{3} V_0$$

$$V_L = \frac{1}{3} V_0$$

Time for up transition

$$= (V_U - V_L) \cdot \left( \frac{2RC}{V_{in}} \right)$$

Time for down transition

$$= (V_L - V_U) \cdot \left( \frac{-2RC}{V_{in}} \right)$$

$$\left. \begin{array}{l} \text{Time for up transition} \\ \text{Time for down transition} \end{array} \right\} \text{Period, } T = \frac{4RC}{V_{in}} (V_U - V_L) = \frac{4RCV_0}{3V_{in}}$$


$$\Rightarrow \text{Frequency } f = \frac{1}{T} = \frac{3V_{in}}{4RCV_0} = \frac{3}{4 \times 10^5 \times 5 \times 10^{-9}} \frac{V_{in}}{V_0} = 150 \frac{V_{in}}{V_0} \text{ here.}$$

CHAPTER 3 BAD CIRCUITS

- Adj. clamp: no current limit on diode.
- AC x10 amp: no path for bias current to + input.
- Generator: no drift protection on integrator - needs large resistor.
- Current source: circuit here is a current limited voltage source.
- DC amplifier: wrong input polarities
- 200 mA current source: zener circuit will not provide enough current should replace 200Ω with < 50Ω.
- Op amp output stage: must bias the - input at a voltage near the quiescent point of the first stage output (7.5V).
- Schmitt trigger: wrong input polarities.
- +15V regulator: op amp output has to be 0.6V above V<sub>+</sub>.
- x10 Audio amp: output quiescent point is 0V, can't swing negative
- DC Amplifier: Z<sub>in</sub> of buffer stage = 1K severely loads range divider. Should use non-inverting configuration
- Zero crossing detector: unprotected input (!)
- +15V regulator: V<sub>+</sub> is too low.






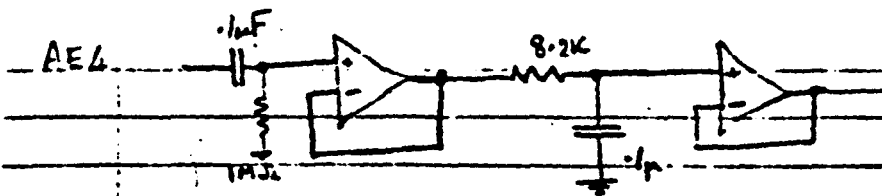

$$RC = \frac{1}{2\pi \cdot 2K} = 8 \times 10^{-3}$$

$$R = \frac{8 \times 10^{-3}}{1 \times 10^{-6}} = 8 \times 10^3$$


AE5:

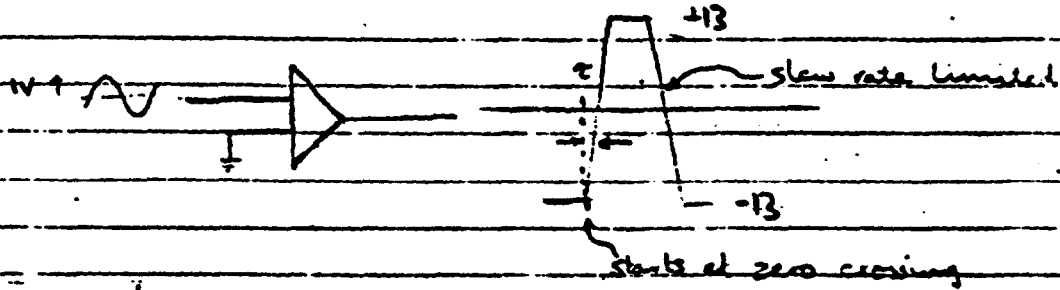

$$\tau = \frac{13V}{5V/\mu s} = 26 \mu s$$

( $1KHz$  sine wave slews at  $2\pi Af V_s^{-1} = 2\pi \cdot 1 \cdot 10^3 V_s^{-1}$   
 in  $26\mu s$  input has risen  $2\pi \cdot 10^3 \times 26 \times 10^{-6} V = 170 \times 10^{-3} V = 170mV$ )

AE6. a)

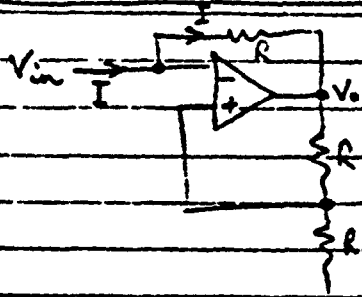


$$V_{in} = \frac{V_o}{2} \quad (1)$$

$$I = \frac{V_{in} - V_o}{R} = \frac{V_{in} - 2V_{in}}{R} = -\frac{V_{in}}{R}$$


$$Z = \frac{V_{in}}{I} = -R$$

b)  $\frac{V_o}{2} < V_{in} < \frac{V_o}{2}$  indicated (from 1)

AE7

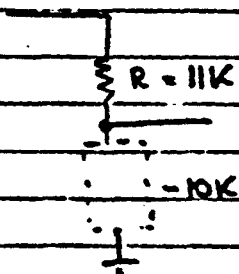


$$G = \frac{-10}{R-10} = -10$$

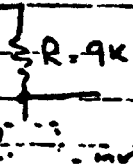

$$G = \frac{-10}{R-10} = +10 ?$$

Consider  $V_i$

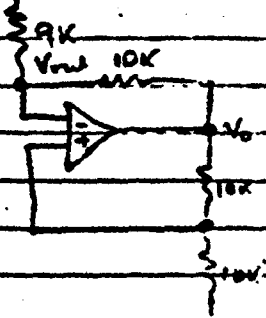

Start at  $V_i = 0$  and  $V_o = 0$   
 $V_o = 0$

$V_i \uparrow$ ,  $V_o \uparrow$  (polarity of op-amp)  
 $\rightarrow V_o \uparrow$  +ve feedback situation  
unstable

Feedback here is the wrong sense for stable operation  
 $V_i = 0$  is a point of unstable equilibrium, from which  
op amp output will move to saturation

End CH. 4 (old 3)

(op amp)

SOLUS