


Physics 364, 2010-09-20, page 1

[First work through quiz question #10 on board.]

Common source of confusion last week: meaning & usefulness of input/output impedance (or resistance).

Suppose Black Box A with output impedance $R_{out,A}$ tries to drive signal V_A to Black Box B which has input impedance $R_{in,B}$. What signal does B see?

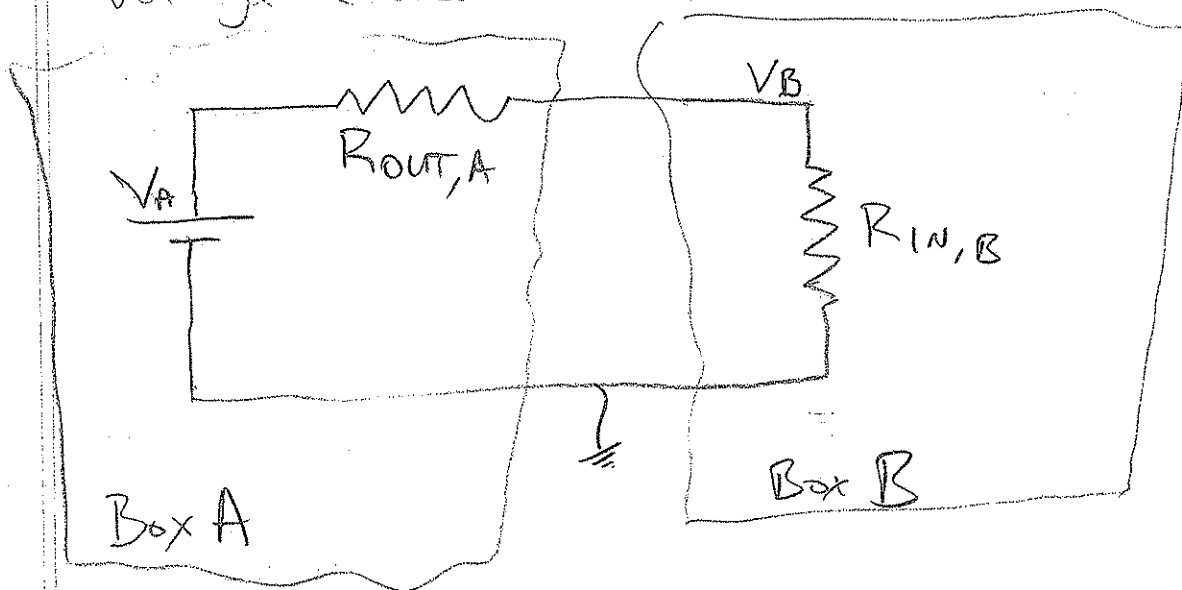Model it as — you guessed it — a voltage divider.




A sends $V_A \equiv V_{thevenin} \equiv V_{oc} \equiv$ A's output with no load connected

$$B \text{ sees } V_B = V_A \cdot \frac{R_{in,B}}{R_{out,A} + R_{in,B}}$$

If $R_{in,B} \gg R_{out,A}$, then $V_B \approx V_A$.

$$\text{i.e. } \lim_{\frac{R_{in,B}}{R_{out,A}} \rightarrow \infty} V_B / V_A = 1$$

Example from Lab 1:

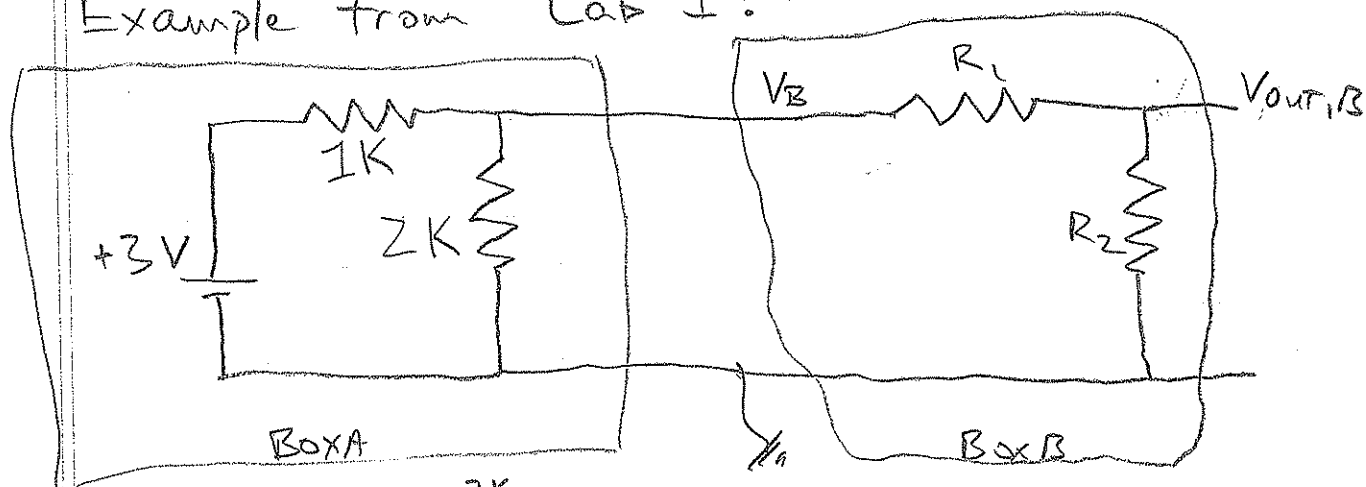

$$V_{THEV,A} = 3V \cdot \frac{2K}{3K} = 2V$$

$$R_{OUT,A} \equiv R_{THEV} \equiv R_{EQ} = 1K // 2K \approx 667\Omega$$

$$R_{IN,B} = R_1 + R_2$$

what B sees is
$$V_B = V_{TH,A} \cdot \frac{R_{IN}}{667\Omega + R_{IN}} = V_{TH,A} \cdot \frac{(R_1 + R_2)}{667\Omega + (R_1 + R_2)}$$

$$V_B = 2V \cdot \frac{(R_1 + R_2)}{667\Omega + (R_1 + R_2)}$$


And
$$V_{out,B} = V_B \cdot \frac{R_2}{R_1 + R_2}$$
 as usual.

If $R_1 = 100K, R_2 = 200K$, then

$$V_B = 2V \cdot \frac{300K}{300.667K} \approx 1.996 V, \quad V_{out,B} \approx 1.33 V$$


If $R_1 = 1K, R_2 = 2K$, then
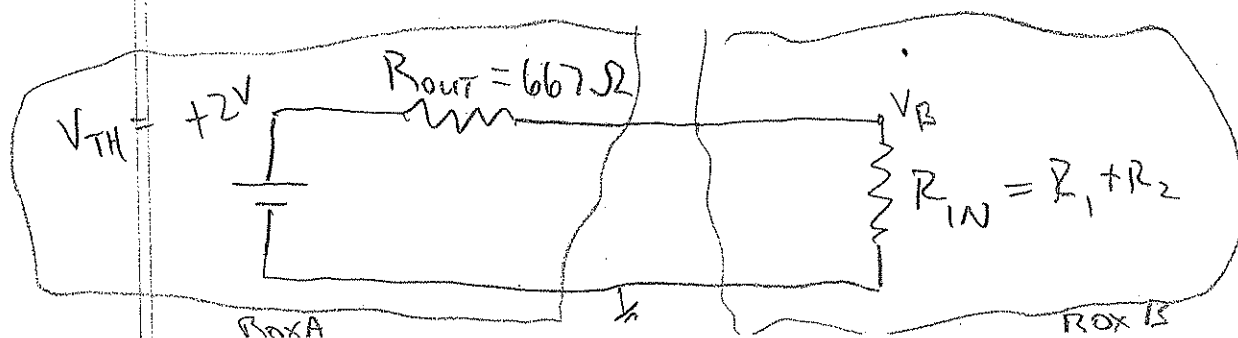
$$V_B = 2V \cdot \frac{3K}{3.667K} \approx 1.64 V, \quad V_{out,B} \approx 1.09 V$$



page 3, 2010-09-20

Computing R_{in} , R_{out} .

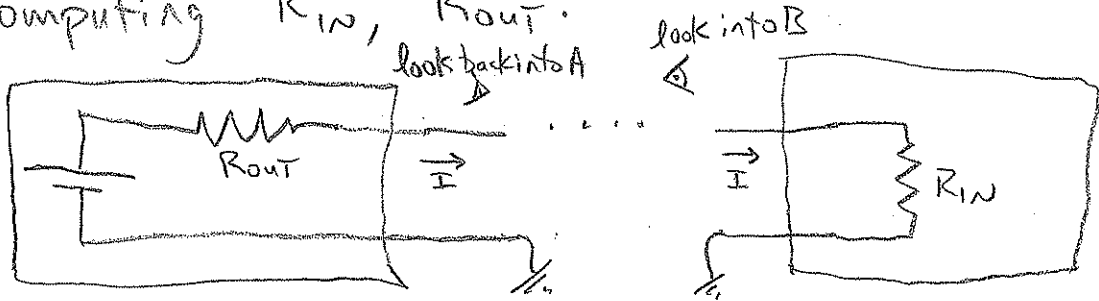

$$\text{Impedance} = \frac{\Delta V}{\Delta I}$$

how much do you have to change I in order to see a given ΔV ?

if you change V , how much does I change?


If A tries to raise V , how much more current must it supply to do so?

If B draws more current from A , how much will V sag?

$$\text{looking back at } A, -\frac{dV_{out}(A)}{dI_{out}(A)} = R_{out}^{(A)}$$


$$\text{looking into } B, \frac{dV_{in}(B)}{dI_{in}(B)} = R_{in}^{(B)}$$

Page 4, 2010-09-20

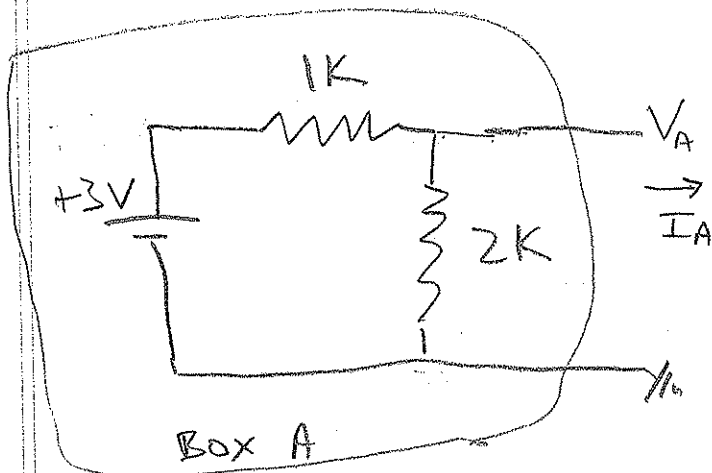

$$\begin{aligned} -\frac{dV_A}{dI_A} &= 667\Omega \\ &= 1K // 2K \end{aligned}$$

$$\frac{dV_B}{dI_B} = R_1 + R_2$$

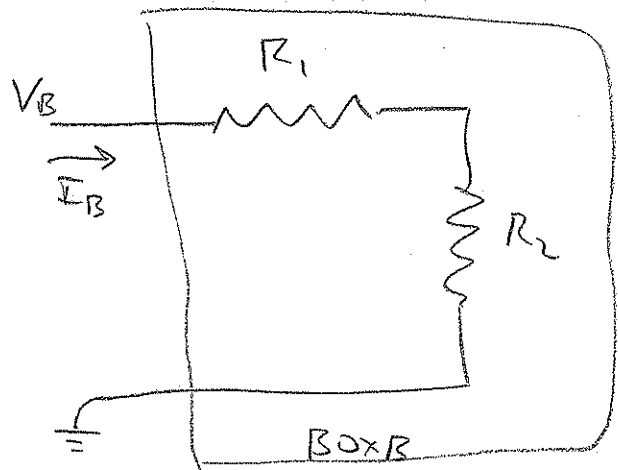

Useful trick for computing R_{out} , R_{in} :

replace all voltage sources with short circuit
replace all current sources with open circuit

evaluate resistance between the two terminals.

(DISCLAIMERS - see text book
only works for ideal, independent sources)

Page 5, 2010-09-20

Generalize Ohm's Law to include phase shifts.

$$V = IR \quad \rightarrow \quad V = IZ$$

Z = impedance, complex quantity


Relationship still linear. Recall two facts about linear systems:

- A linear system driven by $A \cos(2\pi ft)$ responds as $B \cos(2\pi ft + \phi)$, i.e. same frequency, but in general different amplitude & phase
- differentiation is a linear operation

Impedance quantifies response (including phase shift) of a linear circuit as a function of frequency

$$V(t) = V_0 \cos(\omega t) = \operatorname{Re} \{ V_0 e^{j\omega t} \}, \quad j \equiv \sqrt{-1}$$


for a resistor, $Z = R$

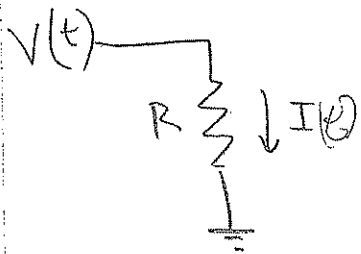

$$\text{If } V(t) = V_0 e^{j\omega t} \\ \text{then } I(t) = (V_0/R) e^{j\omega t}$$

page 6, 2010-09-20

consider a capacitor

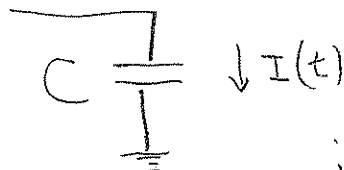
$V(t)$  $\downarrow I(t)$

$$Q = CV$$
$$I = \frac{dQ}{dt} = C \frac{dV}{dt}$$

if $V = V_0 e^{j\omega t}$
then $I = j\omega C V_0 e^{j\omega t} = j\omega C V$

$$V = IZ \Rightarrow Z = \frac{1}{j\omega C}$$

consider an inductor

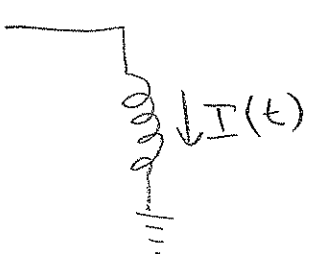$V(t)$  $\downarrow I(t)$

$$V = L \frac{dI}{dt}$$
$$V_0 e^{j\omega t} = L \frac{d}{dt} I_0 e^{j\omega t}$$
$$V_0 e^{j\omega t} = j\omega L I_0 e^{j\omega t}$$
$$V = j\omega L I$$
$$V = IZ \Rightarrow Z = j\omega L$$

Ohm's Law generalized to include R, L, C driven sinusoidally (using complex exponential shorthand):

$$Z = R$$

resistor

$$Z = \frac{1}{j\omega C}$$

capacitor $(|Z| \propto \frac{1}{f})$
D.C. open
high-frequency sh.


$$Z = j\omega L$$

inductor

$(|Z| \propto f)$
D.C. short
high-frequency of

page 7, 2010-09-20

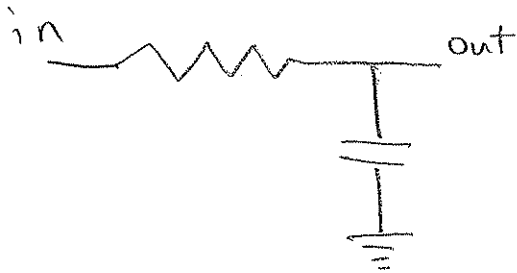New and fascinating sorts of voltage dividers:



$$\frac{V_{out}}{V_{in}} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC}$$

$$\lim_{\omega \rightarrow 0} = 1$$


$$\lim_{\omega \rightarrow \infty} = 0 \quad (\text{with } 90^\circ \text{ phase shift})$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{1 + (2\pi f RC)^2}}$$


"Low pass Filter"


$$\text{at } f = \frac{1}{2\pi RC} \quad \left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}} \quad (\text{"}f_{3dB}\text{"})$$
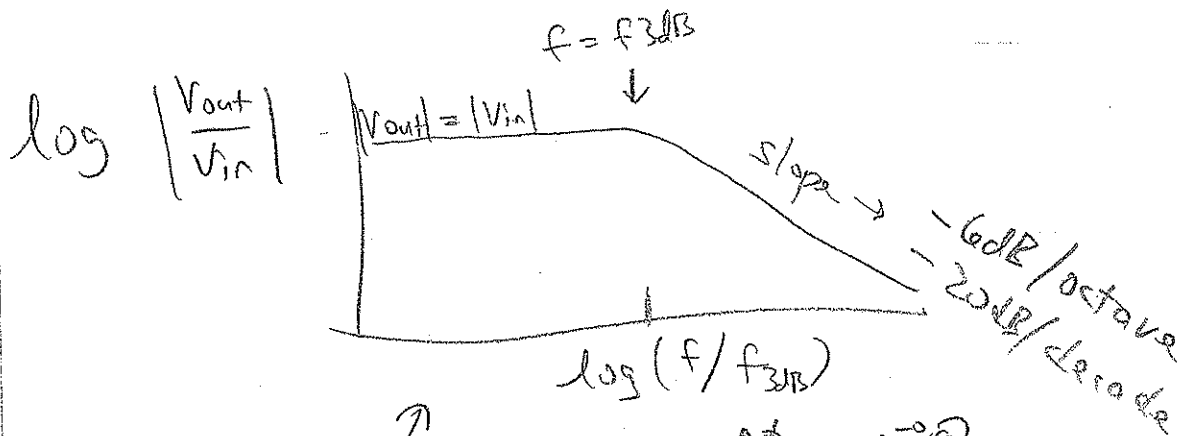
$$\text{at } f \gg \frac{1}{2\pi RC} \quad \lim_{f \rightarrow \infty} \frac{1}{2\pi f RC} = \frac{f_{3dB}}{f}$$



"Bode plot"

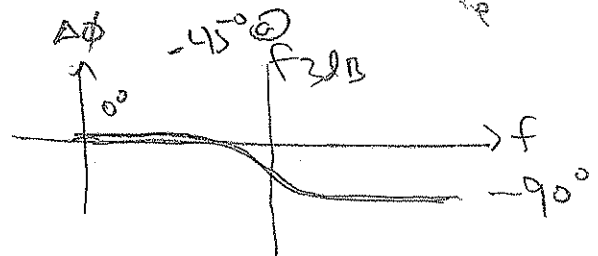

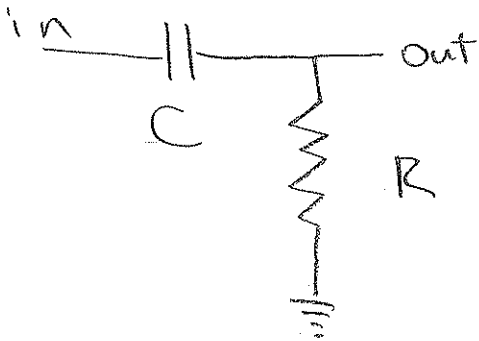

$$\frac{V_{out}}{V_{in}} = \frac{R}{(j\omega C) + R} = \frac{j\omega RC}{1 + j\omega RC}$$

limit $\omega \rightarrow 0 = 0$ (with $+90^\circ$ phase shift)



limit $\omega \rightarrow \infty = 1$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} = \frac{2\pi f RC}{\sqrt{1 + (2\pi f RC)^2}}$$

High pass Filter

at $f = \frac{1}{2\pi RC}$, $\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}}$

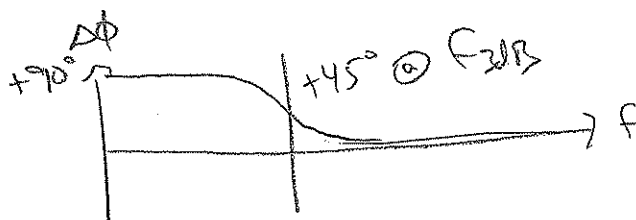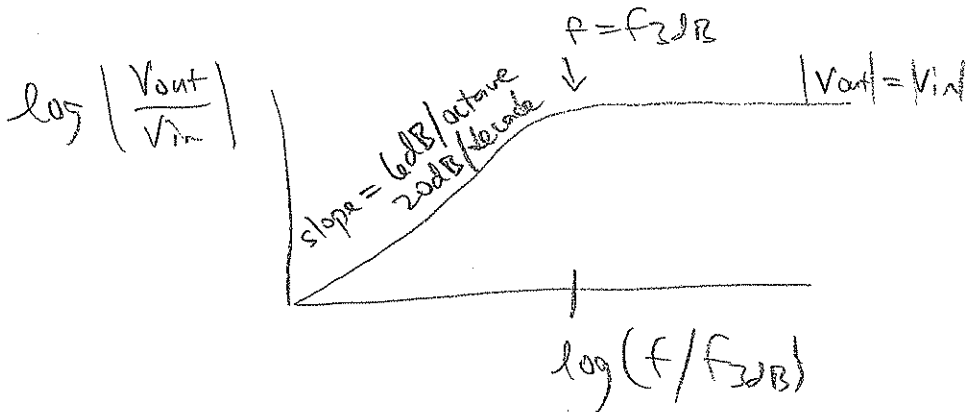at $f \ll \frac{1}{2\pi RC}$, limit $f \rightarrow 0 \rightarrow 2\pi f RC = \frac{f}{f_{3dB}}$



page 9, 2010-09-20

[Now work through quiz problem #2 on board]

[Now go through Lab 2 LTspice examples]

Next week (Lab #3, HW #3)

will be op amp circuits

read Bagg chapter 7

(and) HH 4.00 through 4.10 (pp 175-188)