
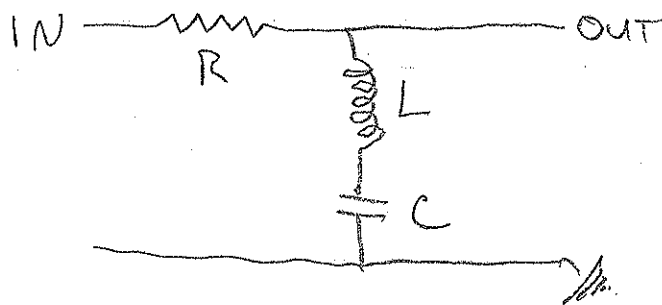


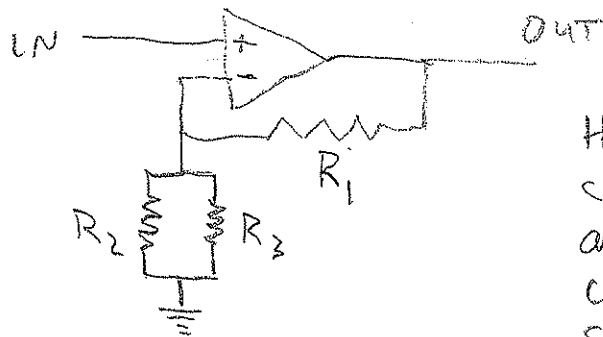① Derive an expression for V_{out} , assuming $V_{in} = \text{Re}\{V_I e^{j\omega t}\}$.




At what frequency $f \equiv \omega/2\pi$ does $V_{out} = 0$?

② Assuming an ideal opamp, calculate V_{out}/V_{in} .




How does your expression change if $R_1, R_2,$ and R_3 are replaced by simple combinations of resistors, capacitors, and inductors?

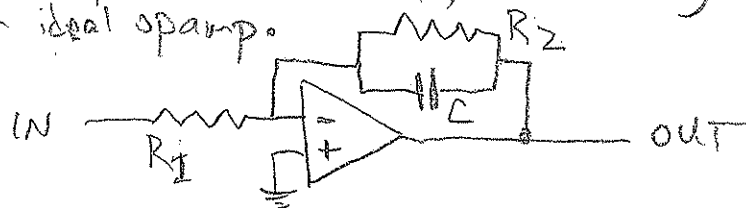③ Derive an expression for V_{out} , assuming $V_{in} = \text{Re}\{V_I e^{j\omega t}\}$. Assume an ideal opamp.



④ For a typical real-life opamp such as the 1741, what happens when the switch is opened (i.e. made non-conducting)? Assume that the switch was initially in the closed (conducting) state. Note the two most relevant opamp imperfections for this circuit.

What would an ideal opamp do?

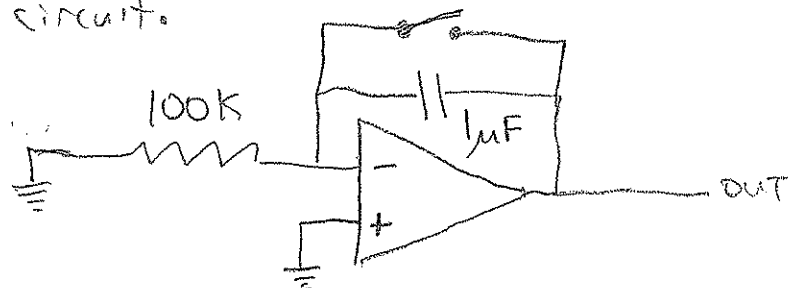

QUIZ #3 SOLUTIONS

PHYSICS 364
2010-10-04

$$\textcircled{1} \frac{V_{out}}{V_{in}} = \frac{j\omega L + \frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1 - \omega^2 LC}{1 - \omega^2 LC + j\omega RC}$$

$$V_{out} = \text{Re} \left\{ \frac{1 - \omega^2 LC}{1 - \omega^2 LC + j\omega RC} \cdot V_I e^{j\omega t} \right\}$$

$$V_{out} = 0 \text{ for } f = \frac{1}{2\pi\sqrt{LC}}$$

$$\textcircled{2} \frac{V_{out}}{V_{in}} = 1 + \frac{R_1}{R_2 // R_3}$$

in more general case, $\frac{V_{out}}{V_{in}} = 1 + \frac{Z_1}{Z_2 // Z_3}$

where $Z = R, j\omega L, \frac{1}{j\omega C}$, etc.

$$\textcircled{3} \frac{V_{out}}{V_{in}} = - \frac{R_2 // \frac{1}{j\omega C}}{R_1} = - \frac{R_2}{R_1 (1 + j\omega R_2 C)}$$

$$V_{out} = \text{Re} \left\{ - \frac{R_2 / R_1}{1 + j\omega R_2 C} \cdot V_I e^{j\omega t} \right\}$$

$\textcircled{4}$ V_{out} would saturate at $\pm V_{supply}$ within seconds, because

$\textcircled{1}$ V_{offset} looks to the opamp as if the (+) input were \pm a few mV

$\textcircled{2}$ Bias current of $\mathcal{O}(100\text{nA})$ has no effect on (+) but through R has same effect on (-) as an input voltage of $I_{BIAS} \cdot R \approx \mathcal{O}(10\text{mV})$.

For an ideal opamp, $V_{out} = 0$ and stays there, assuming capacitor $Q_0 = 0$ (as assured by the switch).