

Physics 364 Quiz: I guarantee everyone will get 100% on this quiz

I Sketch each of these circuits (from memory) and write an expression relating V_{in} and V_{out} .

- a voltage divider
- b RC lowpass filter
- c RC highpass filter
- d RLC bandpass filter

(what is f_0 ?
what is bandwidth?)



- e opamp inverting amplifier
- f opamp integrator
- g opamp follower
- h opamp non-inverting amp
- i what are R_{in} of e and f?
- j BJT emitter follower
- k BJT common emitter amp
- l BJT pushpull buffer
- m opamp trick to cure f's crossover distortion

II What are the basic rules that allow you to analyze most active-mode BJT circuits?

- a names of 3 terminals
- b two currents related by factor β
- c two terminals behaving like a forward-biased diode
- d equation for I_x vs. V_{yz}

III What is the significance of the expression $25\text{mV}/I_c$?