

Bill Ashmanskas, Physics 364 Lab 1, 2010-09-09


Lab partner: Jose Vithayathil

Part 1: using the multimeter

- picked out 1 resistor each from 1Ω , 27Ω , $1K$, $12K$, $330K$ drawers
- HP34401A multimeter, resistance mode.
 - (not sure what Ω 2W vs. Ω 4W means. should look this up in manual at some point.)
- using banana-lead cables with handy banana-to-alligator clip adapters.
 - open circuit \rightarrow "OVLD MOHM"; short circuit $\rightarrow \approx 0.03\Omega$
- measure 1.03Ω (drifts slowly down from ≈ 1.04 to ≈ 1.02 -- probably stray capacitance discharging), 27.0Ω , 989Ω , $11.8K$, $331M$
 - all well within quoted 5% manufacturer tolerance
- line up resistors with stick gold stripes on RHS for easy reading.
 - brown black gold $\rightarrow 1\ 0\ E-1 = 1.0\Omega$; RHS gold stripe $\rightarrow 5\%$ tolerance
 - http://en.wikipedia.org/wiki/Electronic_color_code
 - red violet black $\rightarrow 2\ 7\ E0 = 27\Omega$
 - hard to tell red from orange -- no fun to grow old -- bring reading glasses next time
 - brown black red $\rightarrow 1\ 0\ E2 = 1K$
 - brown red orange $\rightarrow 1\ 2\ E3 = 12K$
 - orange orange yellow $\rightarrow 3\ 3\ E4 = 330K$
- OK, now we'll check Ohm's Law (Yawn?) for these resistors.
 - Aha -- I need my breadboard.
 - Might as well start off with good habits. Use red banana-lead cable to connect red "+" output of +25V supply to red Va; black ("COM" = common \equiv ground) for ground; use little red & blue busses for power distribution, to give me an

excuse to get to know the breadboard

- Work downward from 330K to 1Ω : **330K, 12K, 1K, 27, 1**
 - +1.00V (reads 1.003 but 1% is plenty accurate) to **330K** to ammeter red; ammeter black to ground
 - had to move red cable from volts/ohms to amps jack
 - aha -- 1V/330K $\sim 3\mu A$, absurdly small (though meter reads $2.9\mu A$ -- cool beans). try 25.0V.
 - OK, meter reads $75.3\mu A$. $75e-6 \times 330e3 \approx 24.8 V$ -- Ohm's Law works
 - one more point: $+9.9V \rightarrow 29.8\mu A$ -- check!
 - **12K**: 12V $\rightarrow 1.02mA$ -- check
 - 6V $\rightarrow 0.51mA$ -- check
 - **1K**: 6V $\rightarrow 6.0mA$. 3V $\rightarrow 3.0mA$. good.
 - **27Ω**:
 - power check: $(3V)^2 / 27\Omega \approx 0.3W$, a bit high. start at 1V
 - 1V $\rightarrow 30.8mA$. seems about right. hmm, on second thought, I was expecting more like 37mA. It's as if the resistance were in fact 32.5Ω
 - **1Ω**:
 - now 1V seems way too high, as current would nominally be 1A $\rightarrow 1W$. start with 0.3V $\rightarrow \approx 0.1W$
 - 0.3V \rightarrow measure 45.6 mA. weird! would expect 300mA
 - 0.2V \rightarrow measure 30.8 mA
 - 0.1V \rightarrow measure 16.0 mA.
 - so it's linear, heading toward $\approx (0,0)$, but R looks like $6 \sim 6.5 \Omega$
 - aha! found the HP34401A manual at http://positron.hep.upenn.edu/wja/p364/HP34401A_user_guide.pdf
 - I see on page 216 (specifications), under DC current, a shunt resistance of 5Ω for 10mA and 100mA scales; for 1A,3A scales it is 0.1Ω
 - mystery solved. internal resistance of ammeter is 5Ω
 - Now, for 1Ω I'll explicitly measure the voltage across the two leads of the resistor with next-door multimeter and ad-hoc very long cables. (was fooled at first by meter's being in "rear panel" mode. hah.)
 - $V_{supply} = 100mV \rightarrow 16mA$ of current, 16mV drop across resistor. Ohm's Law is safe!

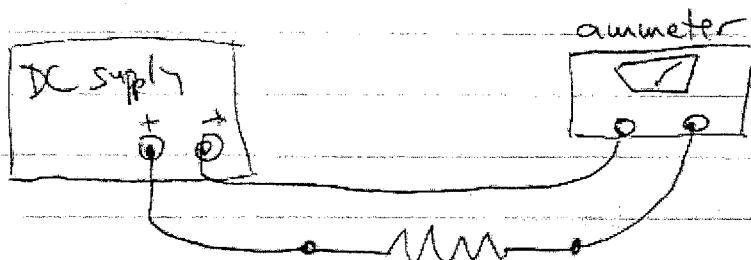


Setup for measuring I vs. V

- supply controls V
- meter reads I
- note 5 Ω shunt resistance of ammeter
on low ($\ll 1A$) current scale

Part 2: voltage divider

Voltage divider

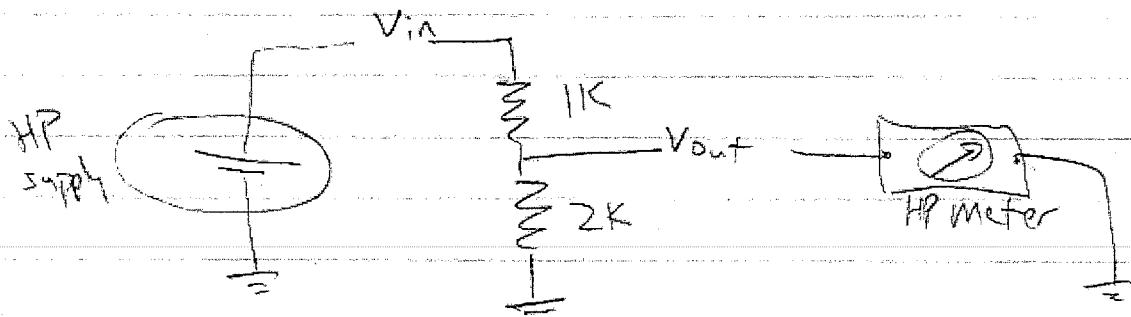

Set $V_{in} = 3.0\text{ V}$ from +25V supply

\Rightarrow measure 2.0 V at meter $\equiv V_{out}$

V_{th} \equiv voltage with $R_{load} = \infty$. Since R_{in} of meter $= 10\text{ M}\Omega \gg R_{th}$ (as we will see below), the meter is directly measuring V_{th} .
 $V_{th} = 2.0\text{ V}$. By calculation, $V_{th} = V_{in} \frac{R_2}{R_1 + R_2}$
 $= 3V \frac{2k}{3k} = 2\text{ V}$. OK.

R_{th} \equiv current with $R_{load} = 0$. Since R_{shunt} of ammeter $= 5\Omega$ (from part I) $\ll R_{th}$ (we'll show) meter is effectively \approx short circuit. Put meter in DC current mode \rightarrow measure 3.0 mA.
 $R_{th} \equiv V_{th}/I_{sc} = 2\text{ V}/3\text{ mA} \approx 670\Omega$.

Calculate: $R_{th} = 1\text{ k} \parallel 2\text{ k} = (2\text{k}(1\text{k})) \parallel 2\text{ k} = \frac{2}{3}\text{ k}$

✓ check

Oops, I meant $I_{sc} \equiv$ current with $R_{load}=0$. $R_{th} \equiv V_{th}/I_{sc}$.

Load divider w/ 100k resistor:

I expect negligible change, as $100\text{k} \gg R_{th} = \frac{2}{3}\text{k}$

predict $2\text{ V} \parallel \frac{(2)(1\text{k})}{100\text{k}} \Rightarrow 2\text{ V} \cdot \frac{100}{100.67} \approx 1.99\text{ V}$


measure \approx 1% drop: $2.008\text{ V} \rightarrow 1.995\text{ V}$, good.

Oops, I meant 10mV drop, or 0.5% drop, not 1%.

Now try 3K resistor. Expect $2V \cdot \frac{3}{3.67} \approx 1.64V$

measure 1.64 V. good

Build 2V

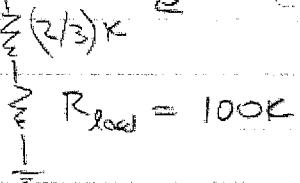

Thévenin
equivalent

*used 680Ω resistor if 1.2K is used
can't have used*


measure 2.009V at top of divider; 1.995V at center.

As expected, same as original circuit.

Now make $R_{load} = 3K$. Measure $V_{out} = 1.64V$.

good

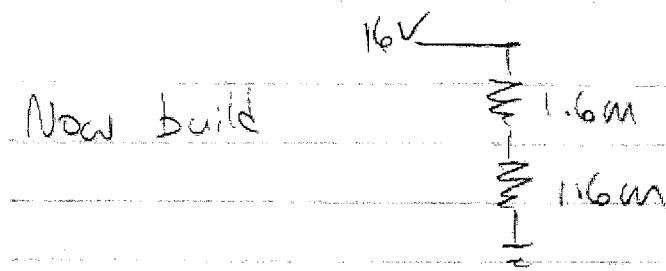The equivalent circuit responds under load in the same way as original, i.e. $I_{out} \propto V_{out}$ for equiv skt $\equiv I_{out} \propto V_{out}$ for original.




I inserted ammeter between lower resistor & ground. Measure $\approx 5 \mu\text{A}$.

$$\text{Calculate } \frac{16V}{3.2M} = 5 \mu\text{A}, \text{ good.}$$

Now measure voltage ("v_{out}") between two resistors, w.r.t. ground. Measure 7.46 volts. Weird - expect 8.0 volts.

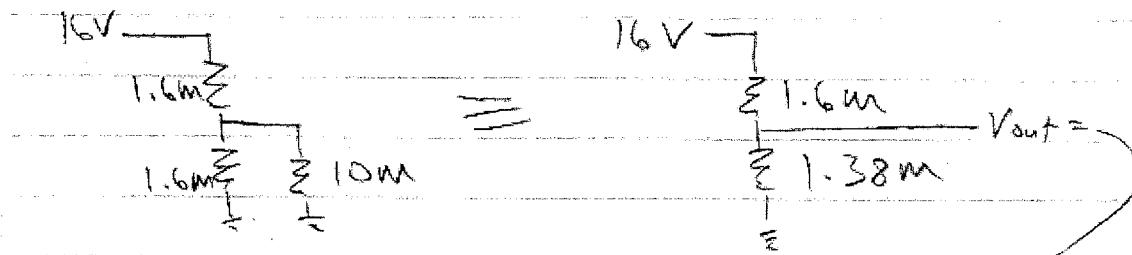Notice meter $R_{in} = 10 \text{ M}\Omega$.



$$16V \cdot \frac{1.38}{1.6 + 1.38} = 7.41V$$

aha!