

Physics 9 — Friday, November 30, 2018

- ▶ Turn in HW10. Pick up handout for HW11, due next Friday.
- ▶ Also pick up your bulb/battery kit again, one per group.
- ▶ Nothing to read for this Monday. We're too big a group to do the Arduino labs this year. But if you want to borrow an Arduino board (+ some related components) and try on your own to program it to blink LEDs, play sounds, etc., that is yet another extra-credit option.
- ▶ For next Wednesday (12/5), you'll read Eric Mazur's ch 27 (magnetic interactions), which will help us to see how to make electricity do useful work (turn a motor, ring a doorbell, etc.)
- ▶ I plan on Monday to hand out the “practice exam” (due on the last day of class, 12/10) which is effectively a take-home portion of your final exam, intended to help you to prepare for the in-class exam (12/17).
- ▶ Full-featured python interpreter in a web browser:
<https://www.pythonanywhere.com/try-ipython/>



(This is how we spent the last 10 minutes of Wednesday's class.)

- ▶ Working with one or two other people, take one bare flashlight bulb, one new **D**-size battery, and one piece of wire.
- ▶ Find four different ways to connect these three objects together such that the bulb lights up.
- ▶ What is the key to making the bulb light up?


Alternatively (your choice) if you have your computer with you, you and your neighbor(s) can build a “virtual” circuit by going to this web link:

https://phet.colorado.edu/sims/html/circuit-construction-kit-dc/latest/circuit-construction-kit-dc_en.html

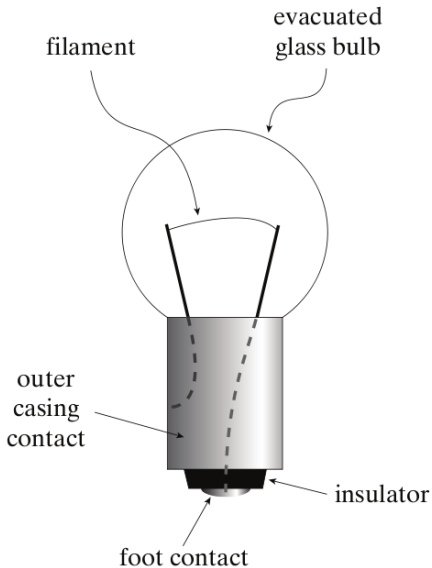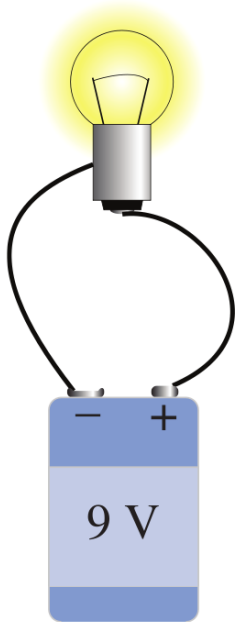If that's hard to type, just go to <https://phet.colorado.edu> and then click “[play with simulations](#)” then “[physics](#)” then “[electricity, magnets & circuits](#)” then “[circuit construction kit: DC](#)” then “[intro.](#)”



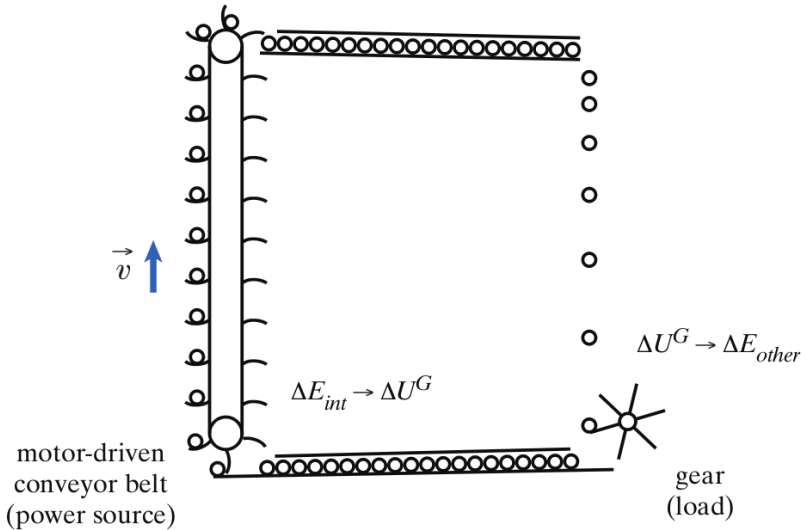(By the way what is the emf (or “voltage”) of a D-cell battery?
It’s much less than 9 volts.)




What in this diagram is analogous to the bulb? Wires? Battery? Voltage? Current? What does a ball represent?

- ▶ Now (for convenience) use sockets to hold the bulb and the battery, and again light the bulb.
- ▶ Do you see where the sockets make their connections to the battery and the bulb?

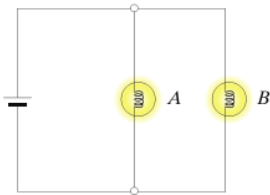-
- ▶ Next, add a switch, so that “closing” (connecting) the switch lights the bulb and “opening” (disconnecting) the switch switches off the bulb. Once it works, sketch a circuit diagram.






Which circuit diagram shows two bulbs connected in series? In parallel? [Click (A)=left diagram, (B)=right diagram.]


- ▶ In which case is the potential difference across bulb *A* equal to the potential difference across bulb *B* **(even if the two bulbs are not identical)**?
 - ▶ In which case does the same current flow through both bulbs **(even if the two bulbs are not identical)**?
-
- ▶ With a friend, try wiring two bulbs in series: how does the brightness of each bulb compare with the single-bulb circuit?
 - ▶ Next try wiring two bulbs in parallel: now how does the brightness of each bulb compare with the single-bulb circuit?
 - ▶ How can you wire a 2nd battery to make the light less wimpy?

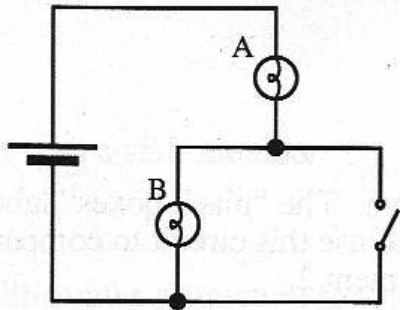If you were to build this circuit, when would bulb A be brighter?



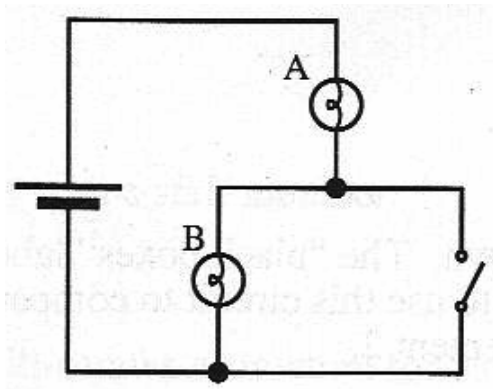
- (A) A is brighter when the switch is open
- (B) A is brighter when the switch is closed
- (C) A is the same brightness in both cases

How does the resistance of bulb B compare with the resistance of a **closed** switch? (A circuit diagram usually shows a switch in its open position, as this one does.)



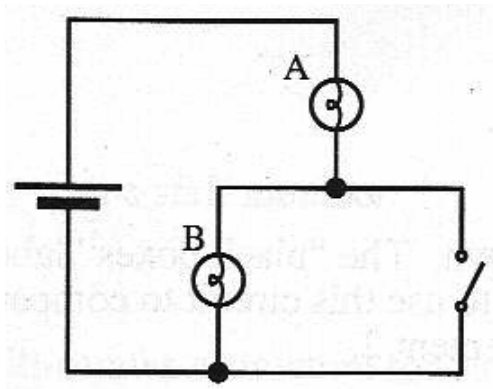
- (A) a closed switch has much smaller resistance than bulb B
- (B) a closed switch has much larger resistance than bulb B
- (C) the resistance of a closed switch is similar to the resistance of bulb B

By the way, what is the resistance of an **open** switch? (Is it very easy or is it very difficult for current to flow through an open switch?)



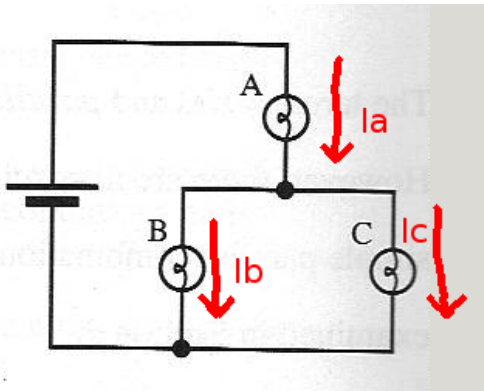- (A) an open switch has a very small resistance, effectively “zero”
- (B) an open switch has a very large resistance, effectively “infinite”

What relationship between I_a , I_b , and I_c does the **junction rule** (a.k.a. "Kirchoff's current rule") allow us to write down?




(A) $I_a + I_b = I_c$

(B) $I_a = I_b + I_c$

(C) $I_a = I_b - I_c$

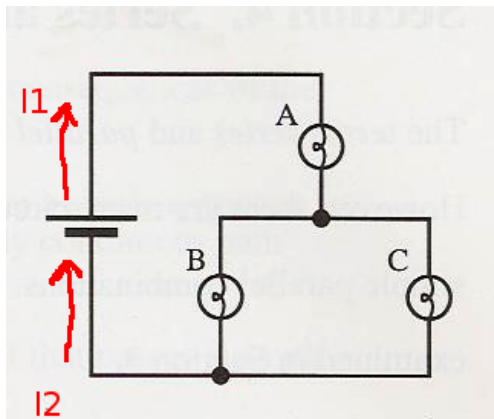
(D) $I_a + I_b + I_c = 0$

In the steady state, how does the current I_1 flowing out of the battery compare with the current I_2 flowing back into the battery?



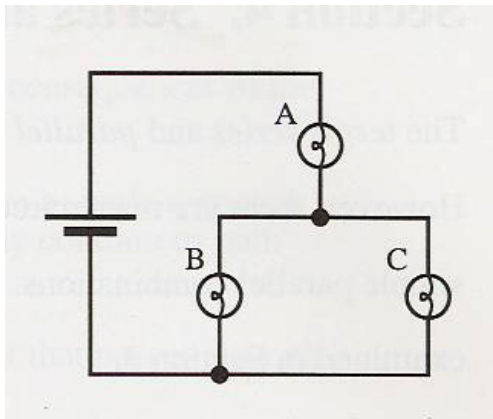
- (A) They are equal.
- (B) I_1 is bigger, because the current is “used up” by the light bulbs.
- (C) They should have the same magnitude, but I_2 should be flowing downward instead.
- (D) You can't tell, because there is a junction where the 3 bulbs meet.

Predict the relative brightness for the three bulbs (assuming the bulbs are identical). Once you predict, feel free to try it — either by combining parts with two other groups or by using the “circuit construction kit: DC” web app!




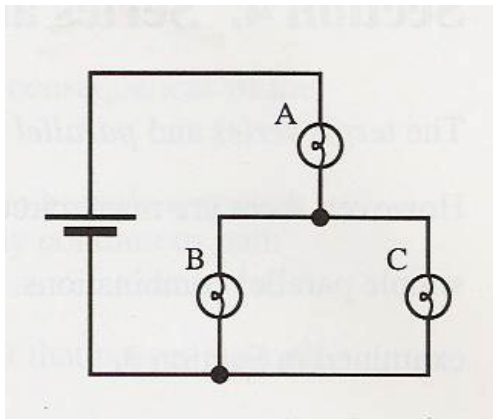- (A) $A < B < C$
- (B) $A < B = C$
- (C) $A = B = C$
- (D) $A > B = C$
- (E) $A > B > C$


You just predicted $A > B = C$ when all 3 (identical) bulbs are present. Now predict what will happen to the brightness of bulbs A and B if bulb C is unscrewed. Once you predict, feel free to try it.



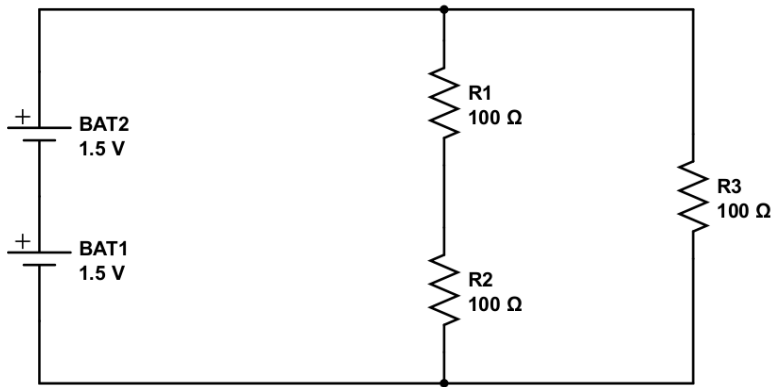
- (A) A and B will both become brighter.
- (B) A and B will both become dimmer.
- (C) A will become brighter, and B will become dimmer.
- (D) A will become dimmer, and B will become brighter.
- (E) The brightness of A and B will not change.



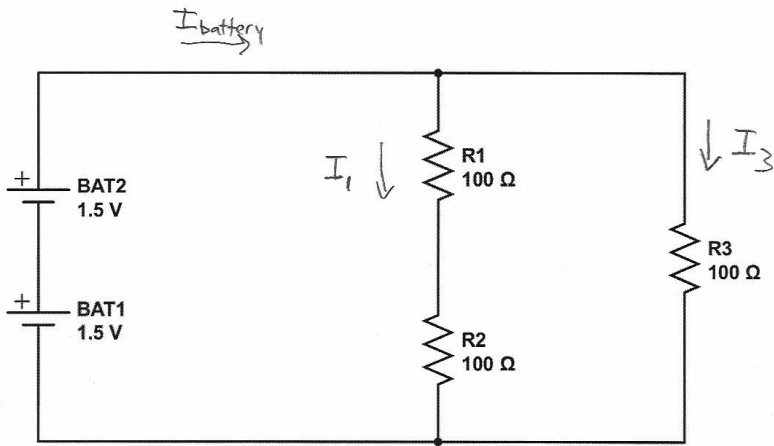
First, identify all of the **branches** in the circuit. For each branch, choose a **reference direction** for the current through that branch. How many branches? How many junctions?



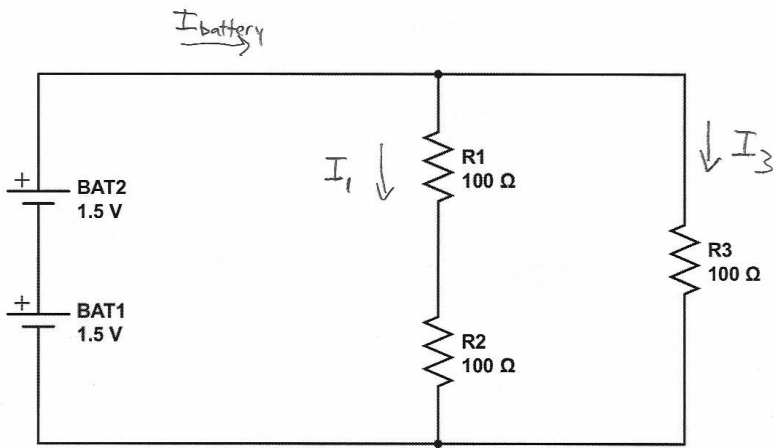
What does the **junction rule** let us write for the junction above R_1 ? In this case, do we get any additional information by applying the junction rule at the junction below R_2 ?





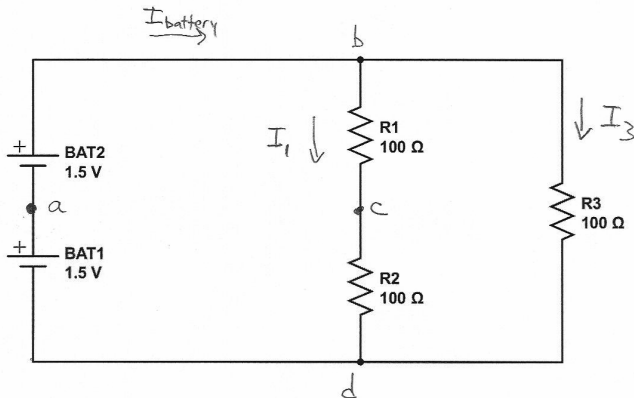There are 3 loops in this circuit. Where are they? Use the loop rule for each one. (Let's go clockwise around each loop — arbitrary choice.) How many of these 3 equations give us new information?




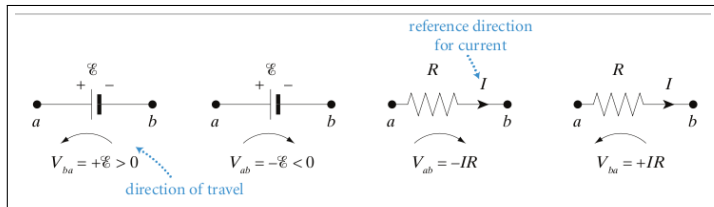Now predict
 V_{ab} , V_{bc} ,
 V_{cd} , V_{bd} ,
 and V_{da} .



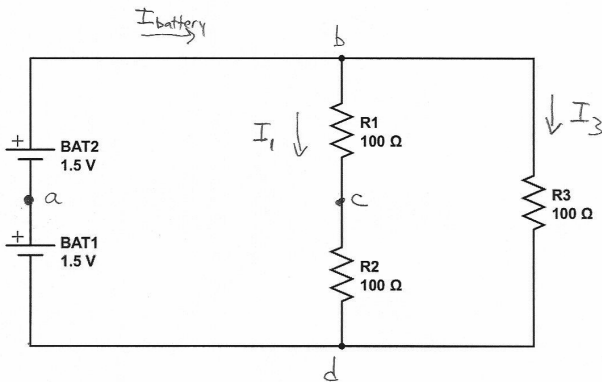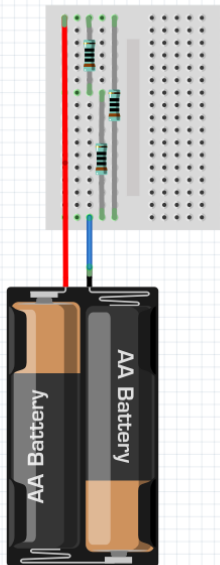


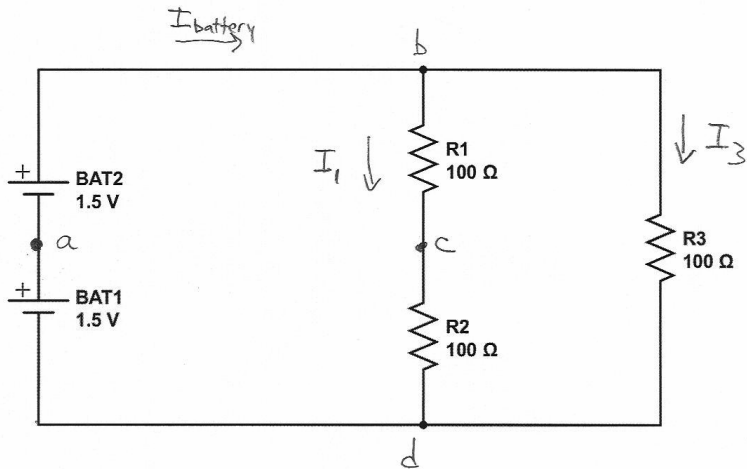
see fritzing.org to draw left, circuitlab.com for right



One more question: What is the power dissipated in each resistor? (Are they all the same, or not?) What is the power supplied by each battery?

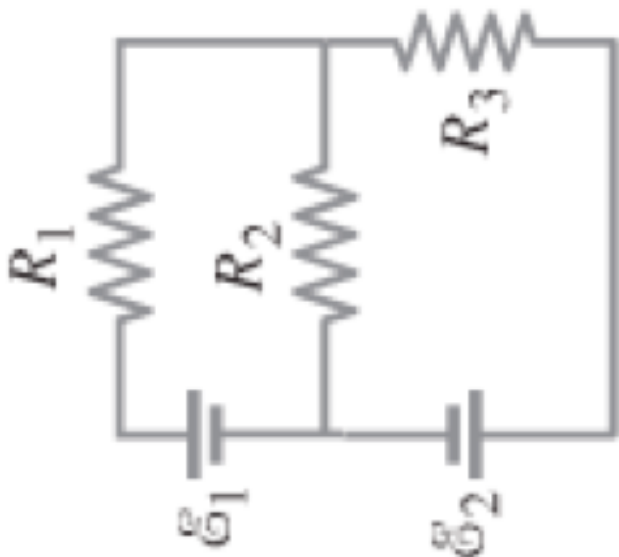Circuits with multiple batteries can be tricky: particularly for getting the signs right. When feasible, I usually try to draw a current going “the conventional way” through each battery, e.g. I_1 going to the left through \mathcal{E}_1 and I_2 going to the right through \mathcal{E}_2 .



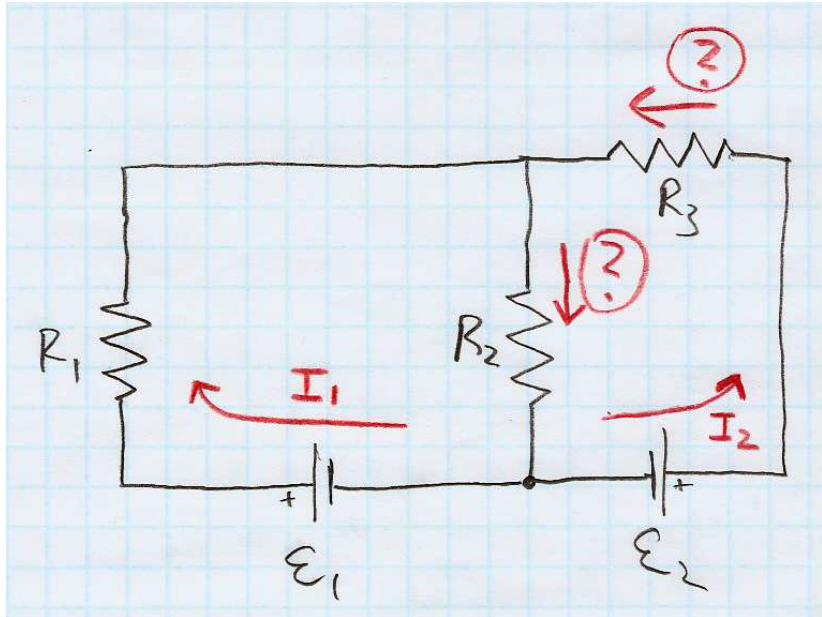

What values can we write for the two ? currents?

What does the loop rule tell us? (3 equations, but 1 is redundant.)

For example, let's plug in

$R_1 = R_2 = R_3 = 10 \, \Omega$, $\mathcal{E}_1 = 2 \, \text{V}$, $\mathcal{E}_2 = 3 \, \text{V}$. Then we get

$$2 \, \text{V} - (10 \, \Omega)I_1 - (10 \, \Omega)(I_1 + I_2) = 0$$

$$3 \, \text{V} - (10 \, \Omega)I_2 - (10 \, \Omega)(I_1 + I_2) = 0$$

If you have two equations in two unknowns (e.g. x and y), you can go to Wolfram Alpha and type (for example)

$$2-10x-10(x+y)=0 \text{ and } 3-10y-10(x+y)=0$$

The screenshot shows the Wolfram Alpha interface. At the top, the URL is [www.wolframalpha.com/input/?i=2-10x-10\(x+y\)=0](http://www.wolframalpha.com/input/?i=2-10x-10(x+y)=0). The search bar contains the input "2-10x-10(x+y)=0 and 3-10y-10(x+y)=0". Below the search bar, the input is repeated: "2-10x-10(x+y)=0, 3-10y-10(x+y)=0". The solution is displayed as $x = \frac{1}{30}$, $y = \frac{2}{15}$. There are buttons for "Approximate form" and "Step-by-step solution".

www.wolframalpha.com/input/?i=2-10x-10(x+y)=0

Search

WolframAlpha computational knowledge engine

2-10x-10(x+y)=0 and 3-10y-10(x+y)=0

Examples Random


Input:

$\{2 - 10x - 10(x + y) = 0, 3 - 10y - 10(x + y) = 0\}$


Solution:

Approximate form Step-by-step solution


$x = \frac{1}{30}, y = \frac{2}{15}$

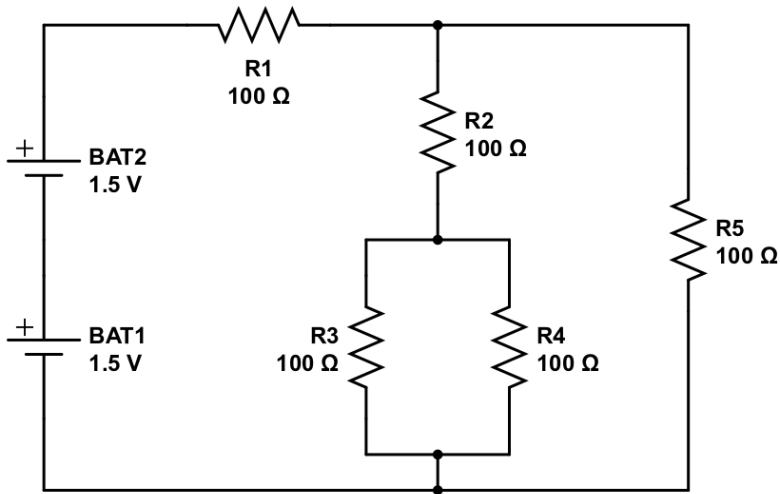

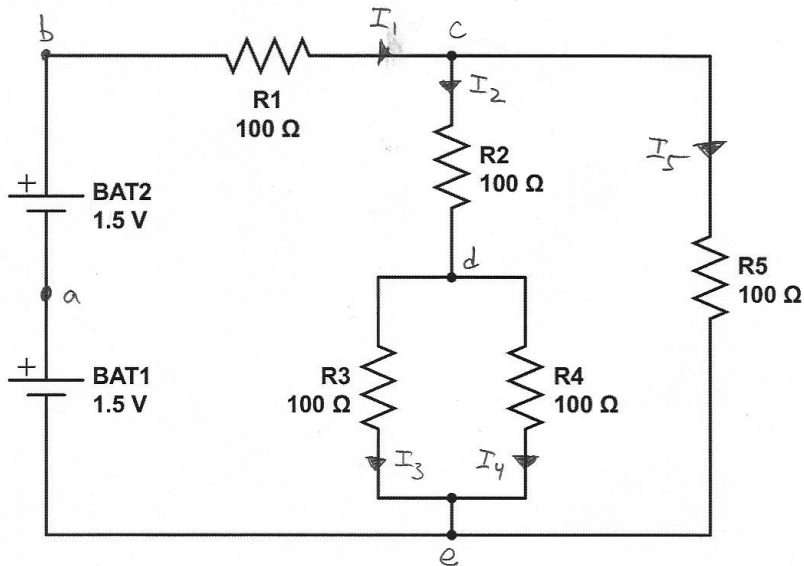This circuit is more complicated. How many branches? Let's choose a reference direction for each branch, choose a name for the current in each branch, and choose a name for all points between which we might want to measure voltage. (Next page.)



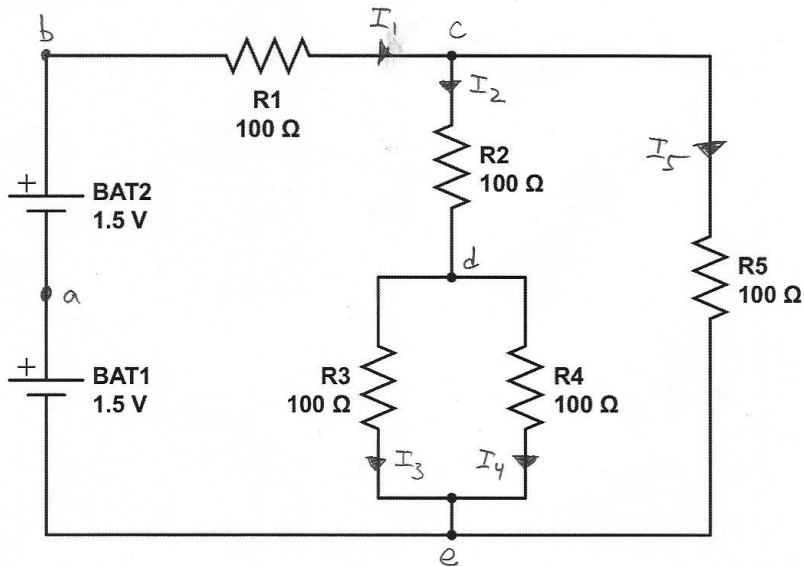What does junction rule let us write at point *c*? Point *d*? Does the junction rule at point *e* tell us anything new?



I count 4 loops. Let's see what the loop rule tells us. Again, one equation will be redundant. We'll just write down the equations, without wasting time to solve them for $I_1 \dots I_5$.

loop rule:

$$\mathcal{E}_1 + \mathcal{E}_2 - I_1 R_1 - I_5 R_5 = 0$$

$$\mathcal{E}_1 + \mathcal{E}_2 - I_1 R_1 - I_2 R_2 - I_3 R_3 = 0$$

$$\mathcal{E}_1 + \mathcal{E}_2 - I_1 R_1 - I_2 R_2 - I_4 R_4 = 0$$

junction rule:

$$I_1 = I_2 + I_5 \Rightarrow \boxed{I_5} = I_1 - I_2$$

$$I_2 = I_3 + I_4 \Rightarrow \boxed{I_4} = I_2 - I_3$$


Plug these in to eliminate I_4, I_5 :

$$\mathcal{E}_1 + \mathcal{E}_2 - I_1 R_1 - (I_1 - I_2) R_5 = 0$$

$$\mathcal{E}_1 + \mathcal{E}_2 - I_1 R_1 - I_2 R_2 - I_3 R_3 = 0$$

$$\mathcal{E}_1 + \mathcal{E}_2 - I_1 R_1 - I_2 R_2 - (I_2 - I_3) R_4 = 0$$

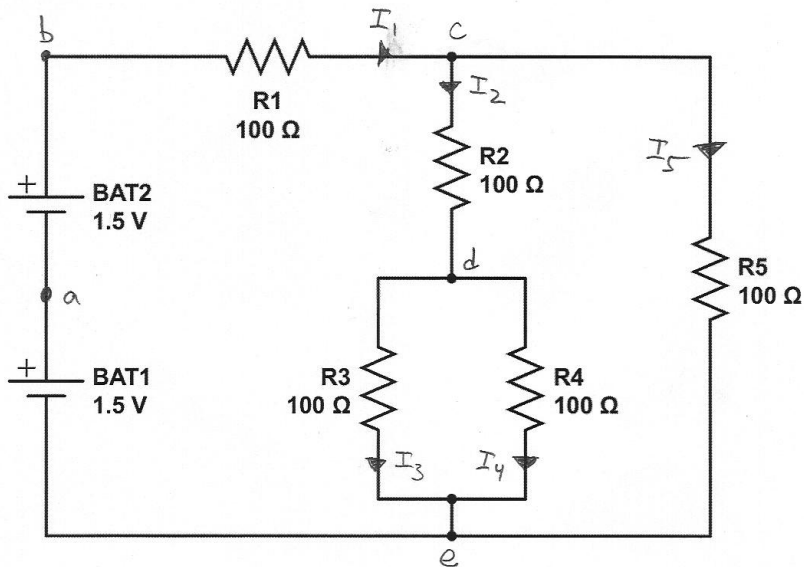Notice that $I_3 R_3 - I_4 R_4 = 0$ is same as
we would get by subtracting the last 2 eqns.



$$I_1 = 0.01875 \text{ A}, I_2 = 0.0075 \text{ A}, I_3 = I_4 = 0.00375 \text{ A}, I_5 = 0.01125 \text{ A}$$

$$I_1 R_1 = 1.875 \text{ V}, I_2 R_2 = 0.75 \text{ V}, I_3 R_3 = I_4 R_4 = 0.375 \text{ V}, I_5 R_5 = 1.125 \text{ V}$$

Physics 9 — Friday, November 30, 2018

- ▶ Turn in HW10. Pick up handout for HW11, due next Friday.
- ▶ Nothing to read for this Monday. We're too big a group to do the Arduino labs this year. But if you want to borrow an Arduino board (+ some related components) and try on your own to program it to blink LEDs, play sounds, etc., that is yet another extra-credit option.
- ▶ For next Wednesday (12/5), you'll read Eric Mazur's ch 27 (magnetic interactions), which will help us to see how to make electricity do useful work (turn a motor, ring a doorbell, etc.)
- ▶ I plan on Monday to hand out the “practice exam” (due on the last day of class, 12/10) which is effectively a take-home portion of your final exam, intended to help you to prepare for the in-class exam (12/17).