

User:Ashmanskas/p364/lab 1 notebook

From LaPET electronics

< User:Ashmanskas | p364

Contents

- 1 Bill Ashmanskas, Physics 364 Lab 1, 2010-09-09
 - 1.1 Part 1: using the multimeter
 - 1.2 Part 2: voltage divider
 - 1.3 Part 3: voltage divider as load for voltage divider


Bill Ashmanskas, Physics 364 Lab 1, 2010-09-09

Lab partner: Jose Vithayathil

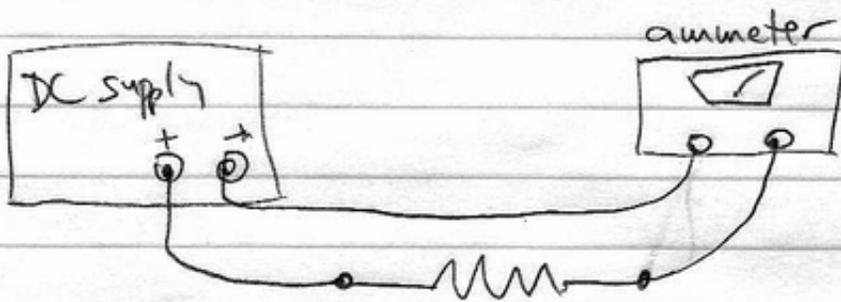Part 1: using the multimeter

- picked out 1 resistor each from 1 Ω , 27 Ω , 1K, 12K, 330K drawers
- HP34401A multimeter. resistance mode.
 - (not sure what Ω 2W vs. Ω 4W means. should look this up in manual at some point.)
- using banana-lead cables with handy banana-to-alligator clip adapters.
 - open circuit \rightarrow "OVL D MOHM"; short circuit $\rightarrow \approx 0.03 \Omega$
- measure 1.03 Ω (drifts slowly down from ≈ 1.04 to ≈ 1.02 -- probably stray capacitance discharging), 27.0 Ω , 989 Ω , 11.8K, 331M
 - all well within quoted 5% manufacturer tolerance
- line up resistors with stick gold stripes on RHS for easy reading.
 - brown black gold $\rightarrow 1\ 0\ E-1 = 1.0\Omega$; RHS gold stripe \rightarrow 5% tolerance
 - http://en.wikipedia.org/wiki/Electronic_color_code
 - red violet black $\rightarrow 2\ 7\ E0 = 27\Omega$
 - hard to tell red from orange -- no fun to grow old -- bring reading glasses next time
 - brown black red $\rightarrow 1\ 0\ E2 = 1K$
 - brown red orange $\rightarrow 1\ 2\ E3 = 12K$
 - orange orange yellow $\rightarrow 3\ 3\ E4 = 330K$
- OK, now we'll check Ohm's Law (Yawn?) for these resistors.
 - Aha -- I need my breadboard.
 - Might as well start off with good habits. Use red banana-lead cable to connect red "+" output of +25V supply to red Va; black ("COM" = common \equiv ground) for ground; use little red & blue busses for power distribution, to give me an excuse to get to know the breadboard
 - Work downward from 330K to 1 Ω : **330K, 12K, 1K, 27, 1**

- +1.00V (reads 1.003 but 1% is plenty accurate) to **330K** to ammeter red; ammeter black to ground
 - had to move red cable from volts/ohms to amps jack
 - aha -- 1V/330K $\sim 3\mu\text{A}$, absurdly small (though meter reads $2.9\mu\text{A}$ -- cool beans). try 25.0V.
 - OK, meter reads $75.3\mu\text{A}$. $75\text{e-}6 \times 330\text{e}3 \approx 24.8 \text{ V}$ -- Ohm's Law works
 - one more point: $+9.9\text{V} \rightarrow 29.8\mu\text{A}$ -- check!
 - **12K**: $12\text{V} \rightarrow 1.02\text{mA}$ -- check
 - $6\text{V} \rightarrow 0.51\text{mA}$ -- check
 - **1K**: $6\text{V} \rightarrow 6.0\text{mA}$. $3\text{V} \rightarrow 3.0\text{mA}$. good.
 - **27 Ω** :
 - power check: $(3\text{V})^2 / 27\Omega \approx 0.3\text{W}$, a bit high. start at 1V
 - $1\text{V} \rightarrow 30.8\text{mA}$. seems about right. hmmm, on second thought, I was expecting more like 37mA. It's as if the resistance were in fact 32.5Ω
 - **1 Ω** :
 - now 1V seems way too high, as current would nominally be $1\text{A} \rightarrow 1\text{W}$. start with 0.3V $\rightarrow \approx 0.1\text{W}$
 - $0.3\text{V} \rightarrow$ measure 45.6 mA. weird! would expect 300mA
 - $0.2\text{V} \rightarrow$ measure 30.8 mA
 - $0.1\text{V} \rightarrow$ measure 16.0 mA.
 - so it's linear, heading toward $\approx (0,0)$, but R looks like $6 \sim 6.5 \Omega$
 - aha! found the HP34401A manual at http://positron.hep.upenn.edu/wja/p364/HP34401A_user_guide.pdf
 - I see on page 216 (specifications), under DC current, a shunt resistance of 5Ω for 10mA and 100mA scales; for 1A,3A scales it is 0.1Ω
 - mystery solved. internal resistance of ammeter is 5Ω
 - Now, for 1Ω I'll explicitly measure the voltage across the two leads of the resistor with next-door multimeter and ad-hoc very long cables. (was fooled at first by meter's being in "rear panel" mode. hah.)
 - $V_{\text{supply}} = 100\text{mV} \rightarrow 16\text{mA}$ of current, 16mV drop across resistor. Ohm's Law is safe!
-




Setup for measuring I vs. V

- supply controls V
- meter reads I
- note 5Ω shunt resistance of ammeter on low ($\ll 1A$) current scale

Part 2: voltage divider

Voltage divider

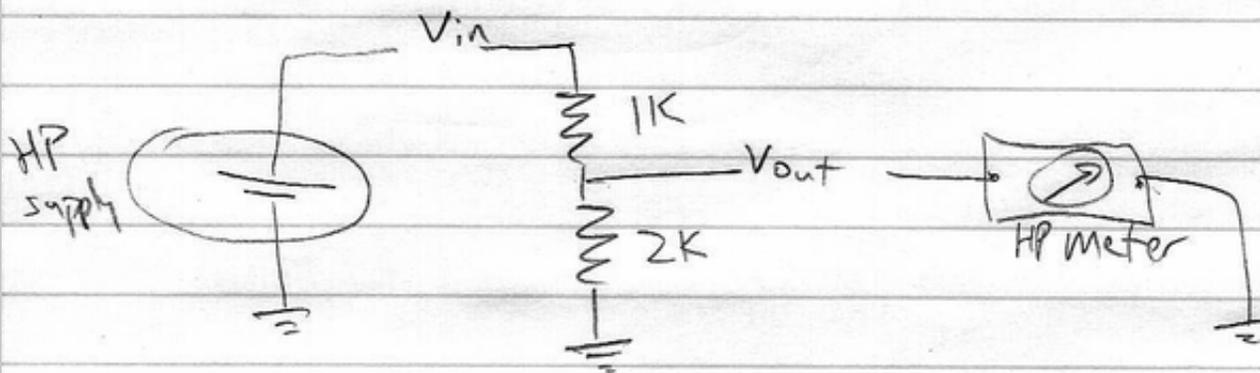

Set $V_{in} = 3.0V$ from $+25V$ supply
 \Rightarrow measure $2.0V$ at meter $\equiv V_{out}$

$V_{th} \equiv$ voltage with $R_{load} = \infty$. Since R_{in} of meter $= 10\text{ M}\Omega \gg R_{th}$ (as we will see below), the meter is directly measuring V_{th} .

$$V_{th} = 2.0\text{ V. By calculation, } V_{th} = V_{in} \frac{R_2}{R_1 + R_2} = 3\text{V} \frac{2\text{K}}{3\text{K}} = 2\text{V. OK.}$$


$R_{th} \equiv$ current with $R_{load} = 0$. Since R_{shunt} of ammeter $= 5\Omega$ (from part I) $\ll R_{th}$ (we'll show), meter is effectively a short circuit. Put meter in DC current mode \rightarrow measure 3.0 mA .

$$R_{th} \equiv V_{th} / I_{sc} = 2\text{V} / 3\text{mA} \approx 670\Omega.$$


$$\text{Calculate: } R_{th} = 1\text{K} \parallel 2\text{K} = (2\text{K} \parallel 2\text{K}) \parallel 2\text{K} = \frac{2}{3}\text{K.}$$

✓ check

Load divider w/ 100K resistor:

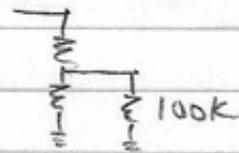

I expect negligible change, as $100\text{K} \gg R_{th} = \frac{2}{3}\text{K}$

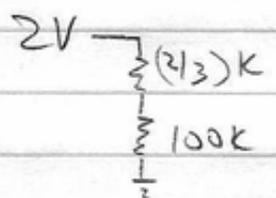predict $2\text{V} \rightarrow$  $\Rightarrow 2\text{V} \cdot \frac{100}{100.67} \approx 1.99\text{V}$

measure $\approx 1\%$ drop: $2.008\text{V} \rightarrow 1.995\text{V. good.}$


Oops, I meant 10mV drop, or 0.5% drop, not 1% .

Now try 3K resistor. Expect $2V \cdot \frac{3}{3.67} \approx 1.64V$

measure 1.64 V. good.

used 680 Ω resistors
could have used 1K // 2K instead

Build 2V

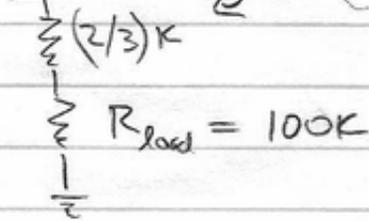

\equiv Thevenin equivalent


measure 2.009 V at top of divider; 1.995 V at center.
As expected, same as original circuit.

Now make $R_{load} = 3K$. Measure $V_{out} = 1.64V$.

good

The equivalent circuit responds under load in the same way as original, i.e. I_{out} vs. V_{out} for equiv ckt \equiv I_{out} vs. V_{out} for original.

Now build

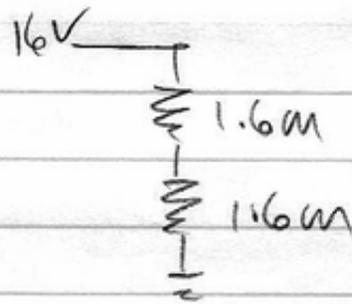


I inserted ammeter between lower resistor & ground. Measure $\approx 5\mu A$.

$$\text{Calculate } \frac{16V}{32m} = 5\mu A. \text{ good.}$$

Now measure voltage ("vout") between two resistors, w.r.t. ground. Measure 7.46 volts. Weird - expect 8.0 volts.

Notice meter $R_{in} = 10m\Omega$.

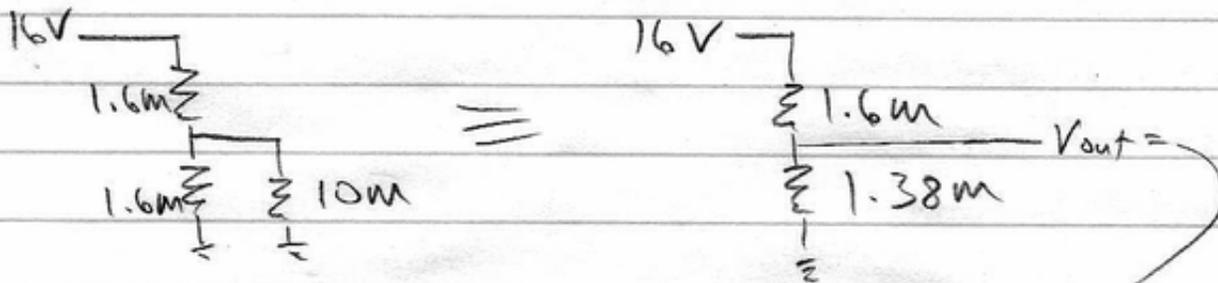

$$16V \cdot \frac{1.38}{1.6 + 1.38} = 7.41V$$

aha!

Part 3: voltage divider as load for voltage divider

Retrieved from "http://positron.hep.upenn.edu/pet/wiki/index.php/User:Ashmanskas/p364/lab_1_notebook"

- This page was last modified on 13 September 2010, at 11:01.