

Physics 364 / 564

Reminder:

Lecture: Mondays only, 2-3:30

Labs: Mondays & Thursdays, 5-9pm

P364
2010-09-13
page 1

$$\vec{J} = \sigma \vec{E}$$


Ohm's Law: $V = IR$ (physics: acceleration between scatters)

Kirchoff: KCL $\equiv \sum I = 0$ into one node
(conservation of charge)

KVL $\equiv \sum_{\text{loop}} \Delta V = 0$
(conservation of energy)

$$\left(\oint \vec{E} \cdot d\vec{\ell} = - \frac{d}{dt} \Phi_B \right)$$


Series

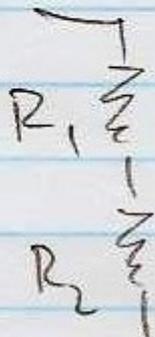

$$\Delta V = IR_1 + IR_2 = I(R_1 + R_2)$$

$$R_{\text{series}} = R_1 + R_2$$

parallel

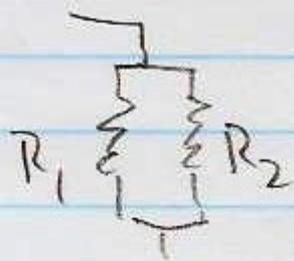

$$I = \frac{\Delta V}{R_1} + \frac{\Delta V}{R_2} = \Delta V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{1}{R_{11}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\Rightarrow R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

shortcuts: $R + r \approx R$


$(R \gg r)$ $R // r \approx r$

$$R // R = \frac{1}{2} R$$


$$R // 2R = (2R // 2R) // 2R = \frac{2}{3} R$$

p364, 2010-09-13, page 2

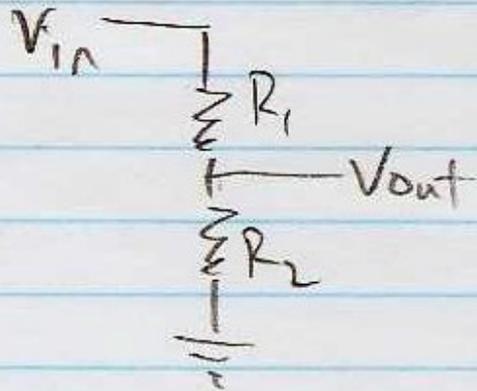voltage divider: see again and again, in various forms


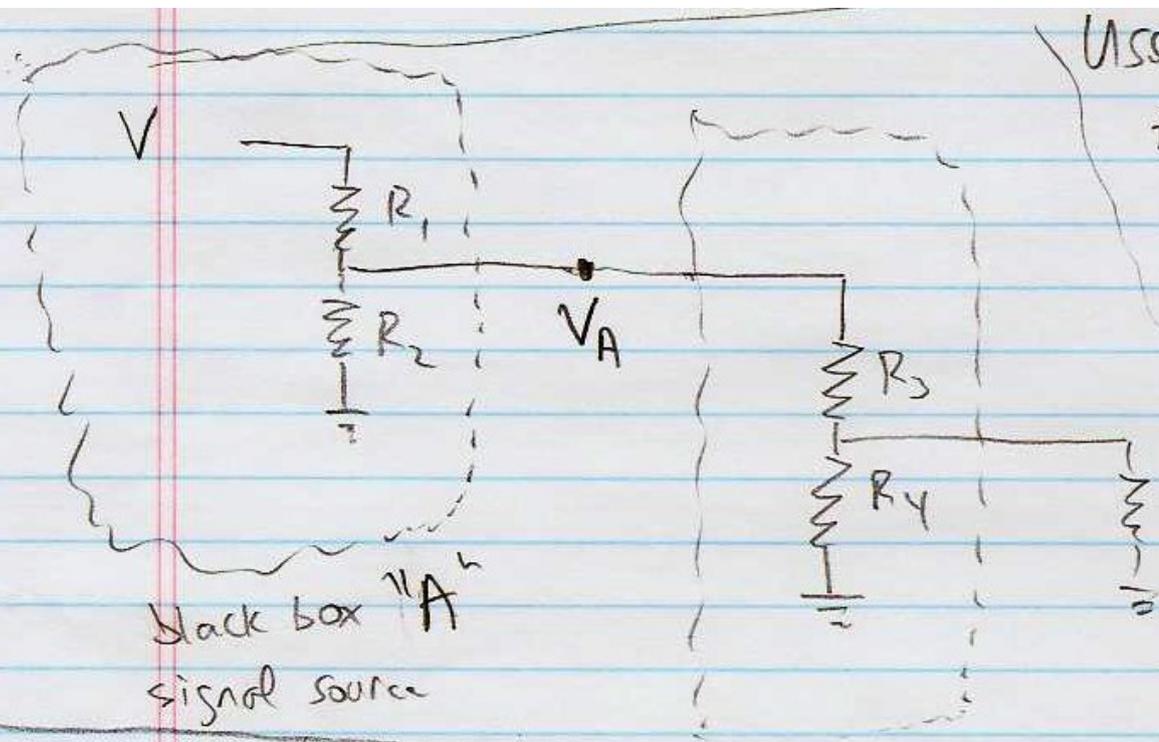
$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2}$$



Use voltage dividers b/c they are what you know so far. More complicated boxes later.

Black box "A" signal source

$R_5 = \text{box B's load}$

Some assumption about R_5 needed to evaluate R_{in}

Some assumption about V (ideal?) needed to evaluate V_{out}

black box load "B"

To A, B looks just like $R_3 + (R_4 // R_5) + \frac{1}{\equiv}$


We say "input impedance" of B is $R_3 + (R_4 // R_5)$

To B, A looks like $R_{th} = R_1 // R_2 + V_{th} = \frac{V R_2}{R_1 + R_2}$

If $R_{in}(B) \gg R_{out}(A)$ then "loading" A with B does not cause A to "droop" / "sag".

(Analogous (opposite) rule for current sources.)

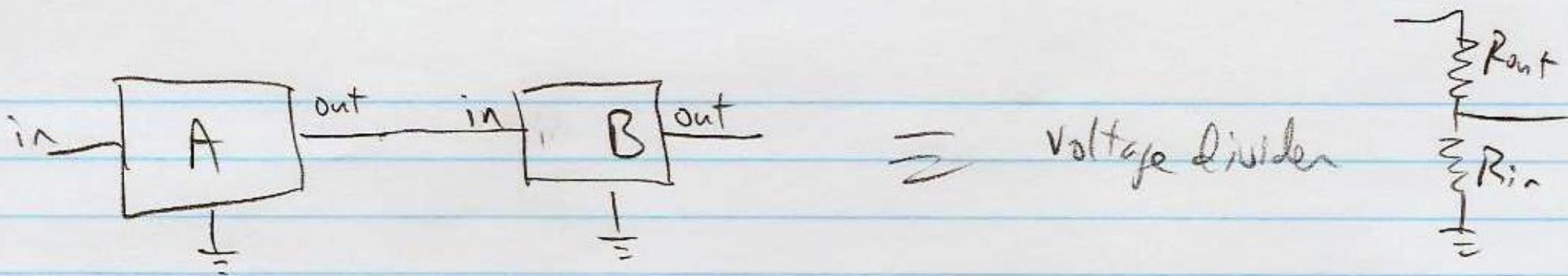→ e.g. you build amplifier to boost a voltage, don't want to lose your voltage gain b/c can't drive load.




When circuit fragment A drives circuit fragment B,
rule of thumb: $R_{out}(A) \ll R_{in}(B)$

e.g. $R_{in}(B) \approx 10 \times R_{out}(A)$

I use $\times 100$ in HW problems for emphasis, but that is often excessive. Depends on acceptable droop.

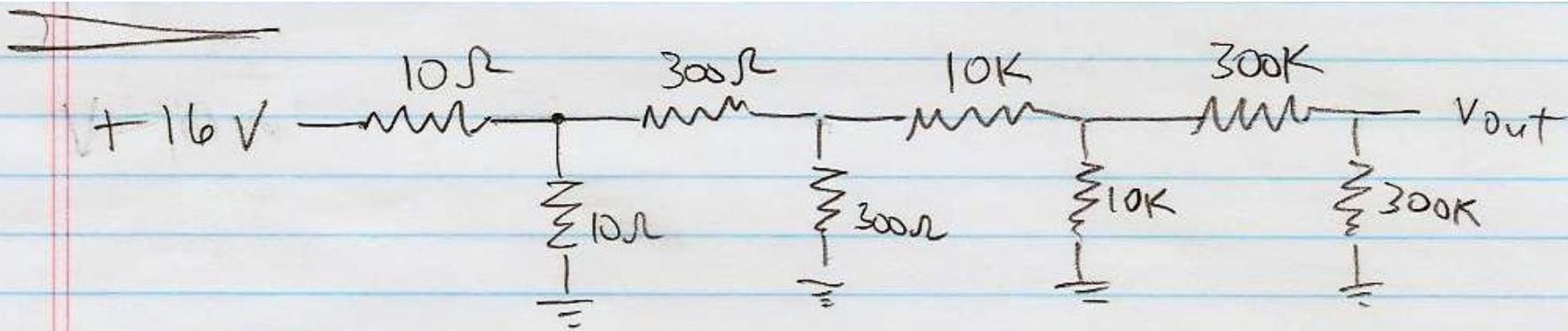
Can design circuit fragments independently if follow rule of thumb.



0.98 volt

What is V_{out} ? (Discuss with neighbor!)

Now what if every resistor is 1K?

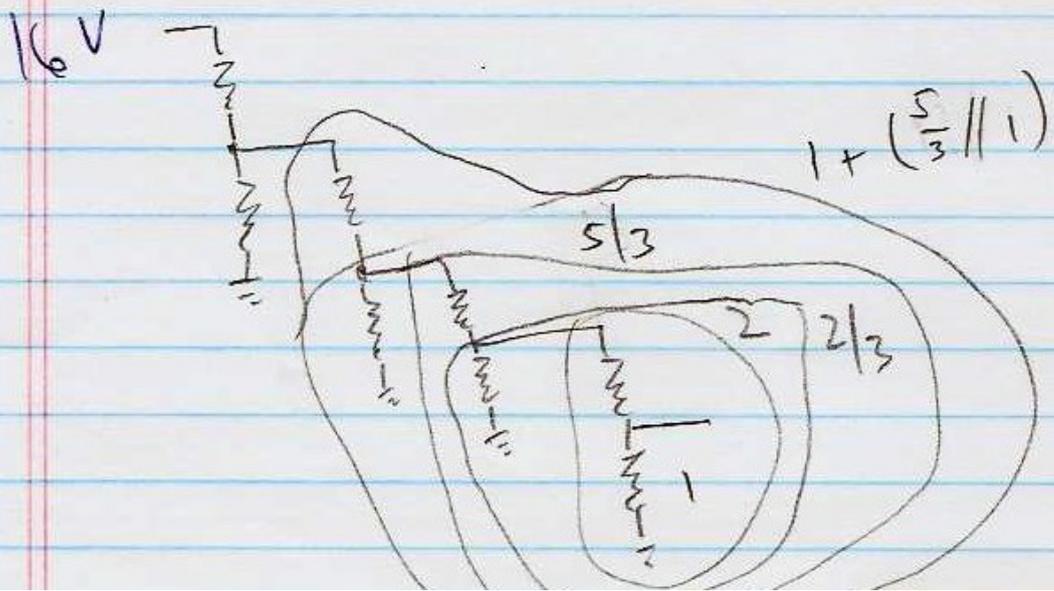


$$\approx 0.47V$$

To determine impedance: change V , measure $\frac{\Delta V}{\Delta I} \equiv R$

extreme case: $\frac{V_{th}}{I_{sc}}$ (compares open circuit w/ short circuit)

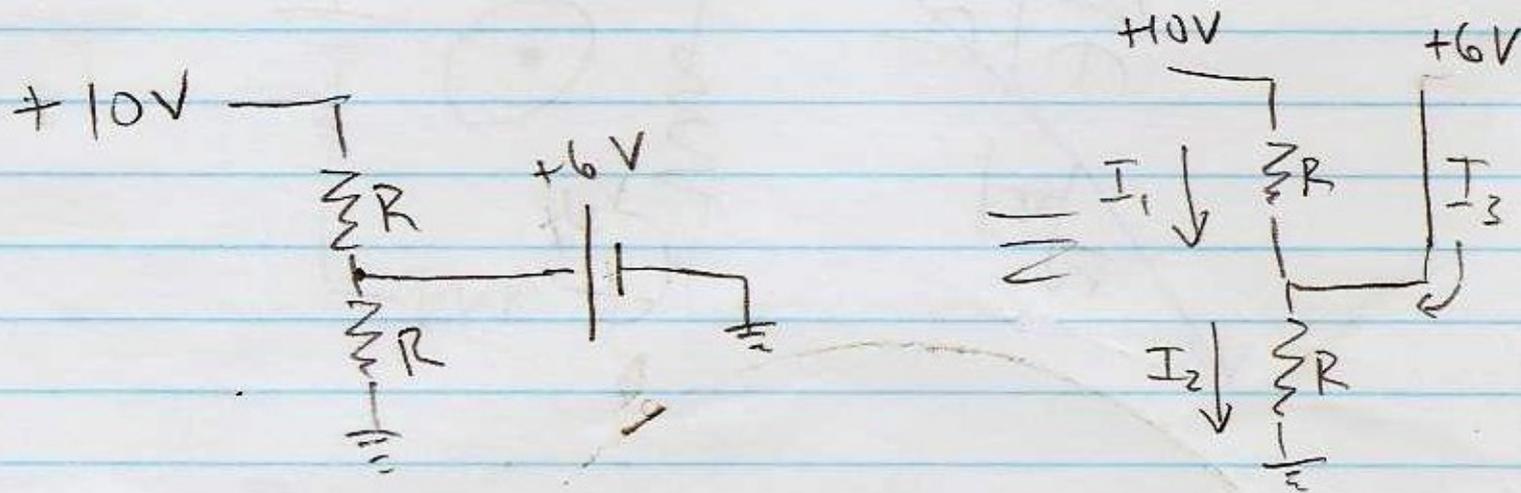We forced V_{out} to be 0 volts, then measured ΔI .



(many ways to draw)

$$I_1 = \frac{10V - 6V}{R} = \frac{4V}{R}$$

$$I_2 = 6V/R$$

$$I_3 = I_2 - I_1 = \frac{2V}{R}$$




after forcing divider output to +6V,

$$\Delta V = 6V - V_{th} = 6V - 5V = 1V$$

$$\Delta I = I_3 - 0 = \frac{2V}{R}$$

$$\Delta V / \Delta I = R/2$$

Same as R_{th} !

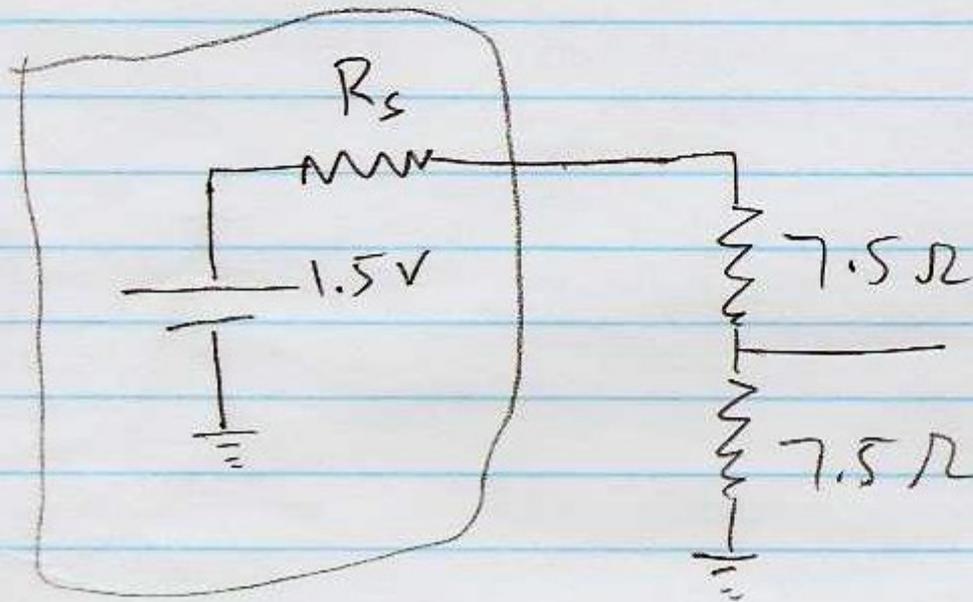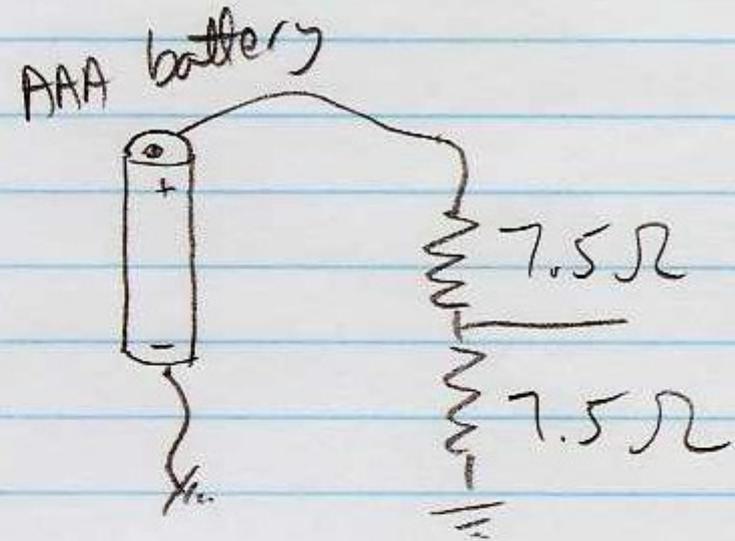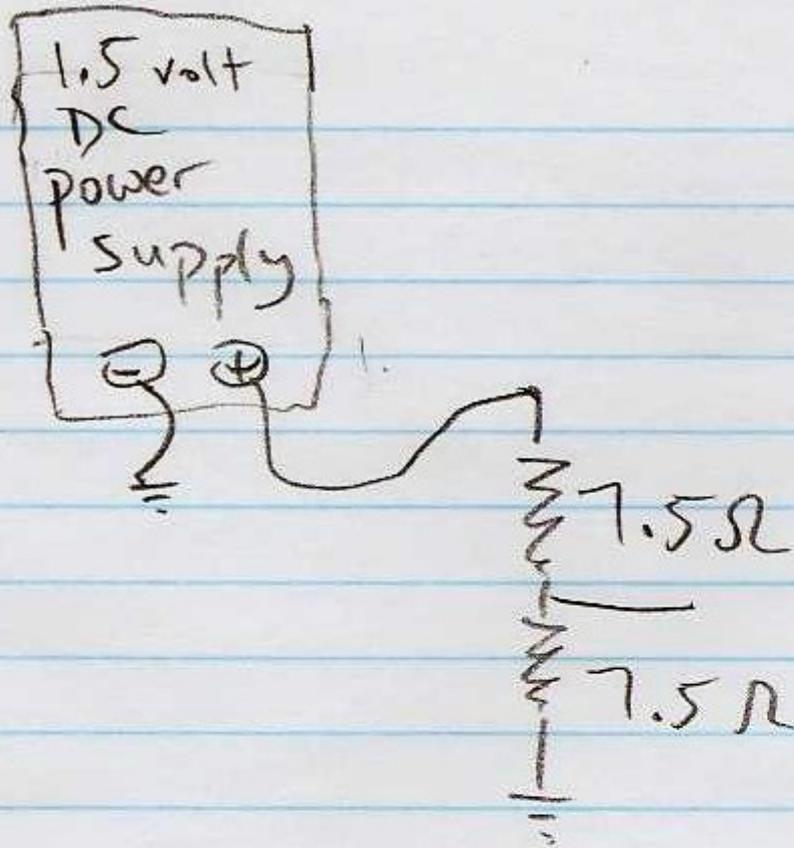


Note:

AAA battery is a bit less weak than I thought. Its internal resistance is about 0.2 – 0.3 ohms, according to a vendor data sheet. So 1.5 ohm would have been a better choice here than 7.5 ohm.


"stiff" voltage source $\approx R_s \ll R_{in}$

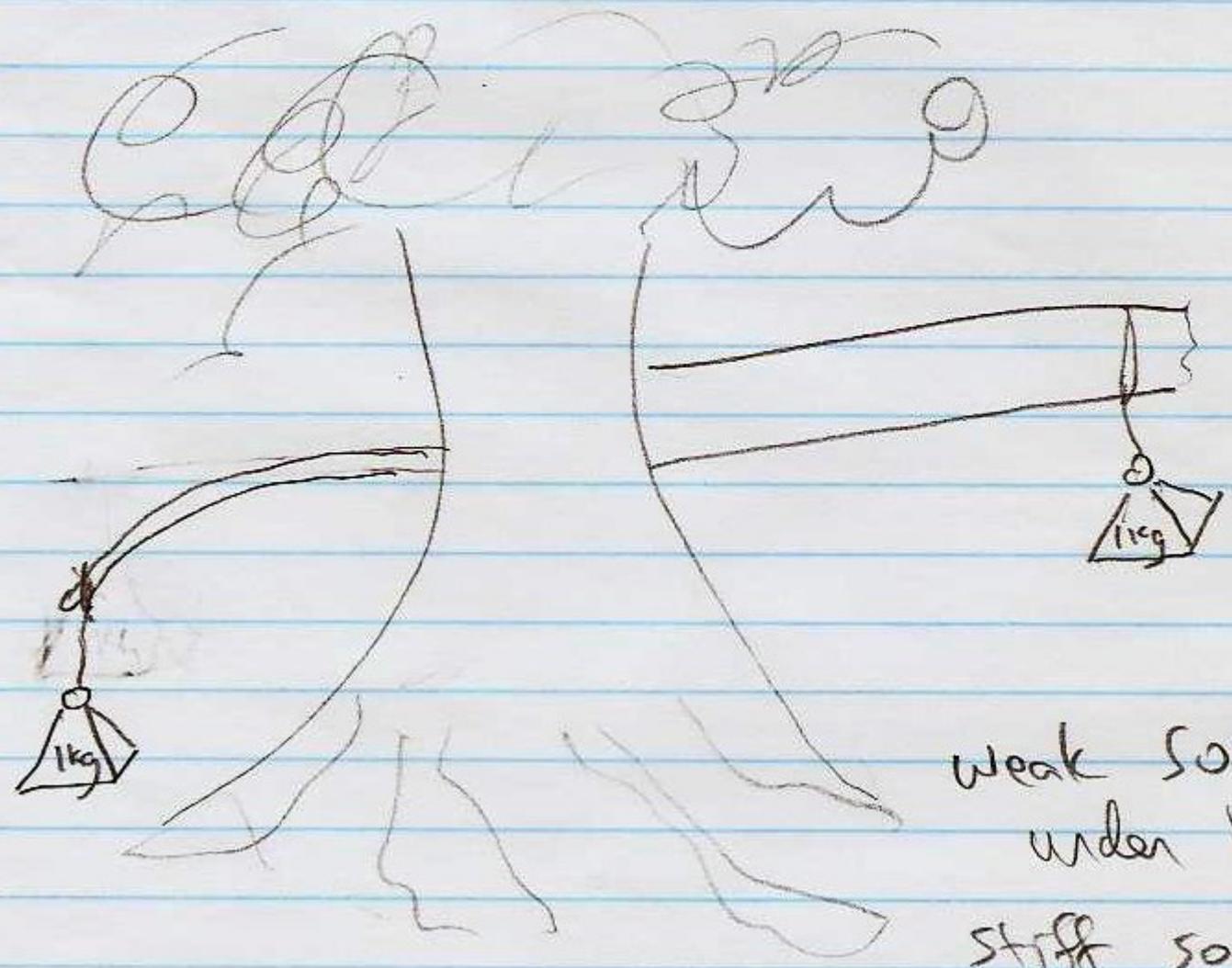"weak" voltage source $\approx R_s \sim R_{in}$



weak source droops/sags under load.

stiff source unchanged

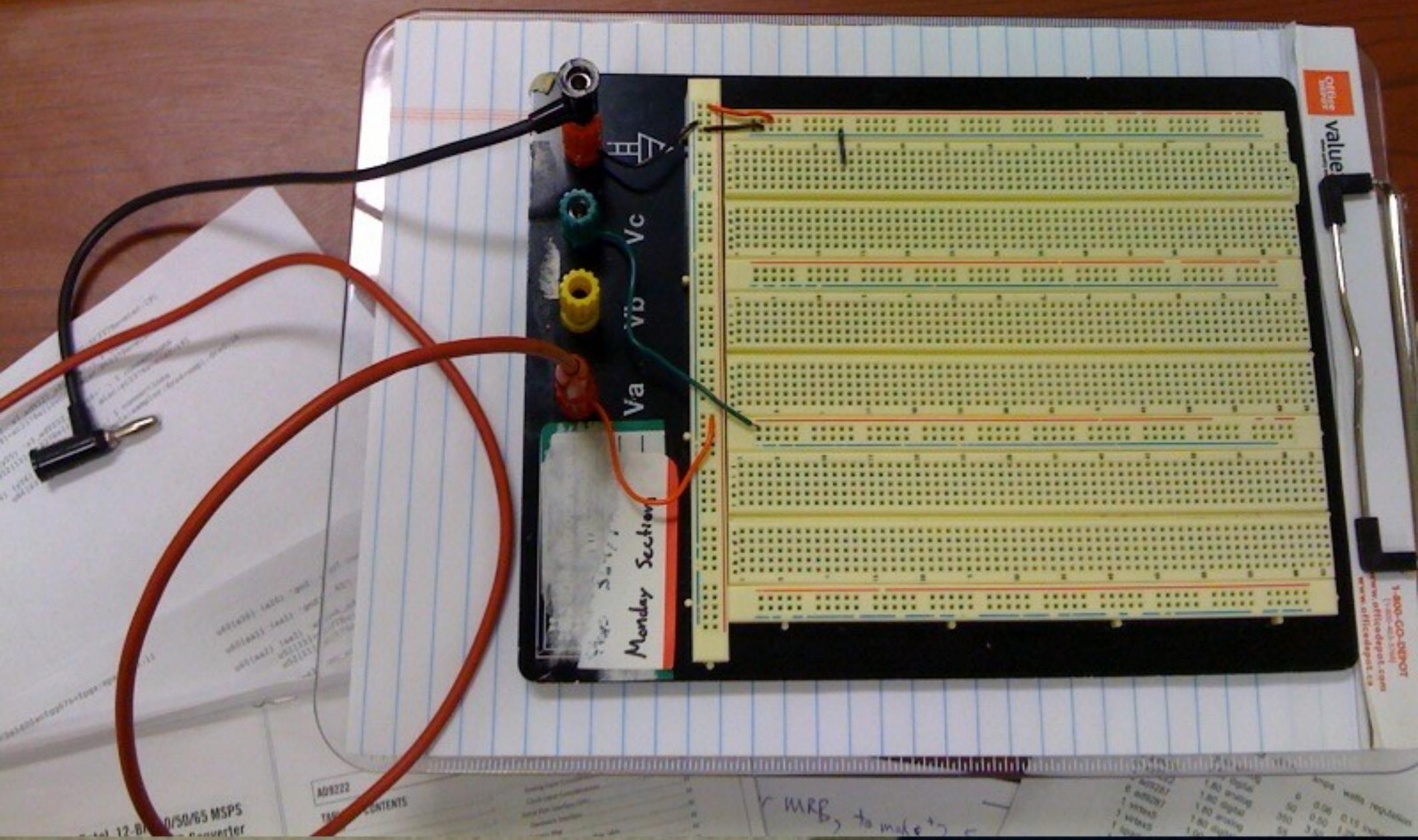

Monday Section

Va Vb Vc

value

1-800-GO-DEPOT
www.officedepot.com

MRE₂ to make +2


Part	Value	Notes
1	1.80 analog	with regulator
2	1.80 digital	
3	1.80 analog	
4	1.80 digital	
5	1.80 analog	
6	1.80 digital	
7	1.80 analog	
8	1.80 digital	
9	1.80 analog	
10	1.80 digital	

- MSP430G2.001
- MSP430G2.001
- MSP430G2.001
- MSP430G2.001

AD9222

CONTENTS

12-Bit 10/50/65 MSPS Converter

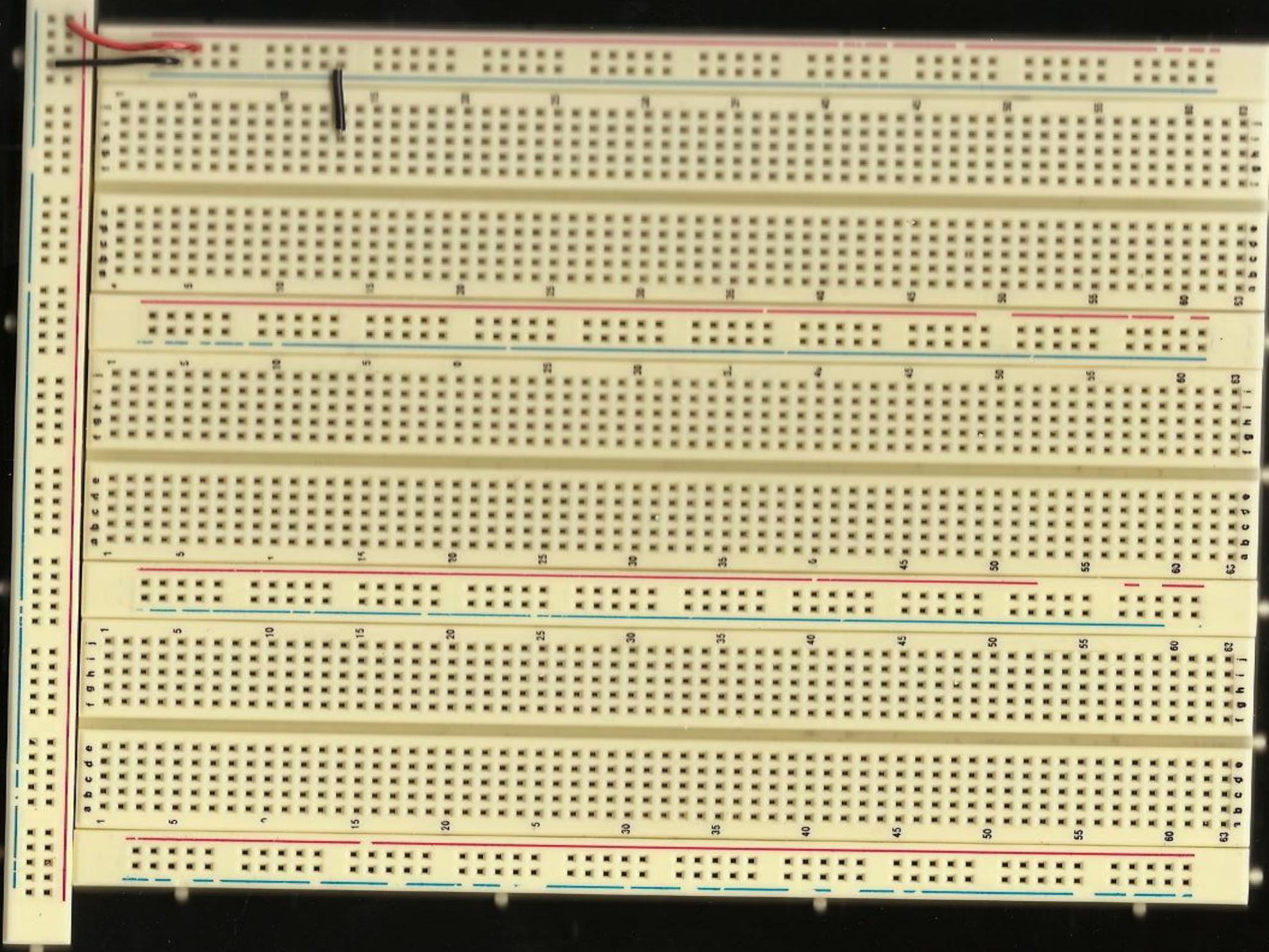

1
5
10
15
20
25
30
35
40
45
50
55
60
65

f g h i j

1
5
10
15
20
25
30
35
40
45
50
55
60
65

f g h i j

1
5
10
15
20
25
30
35
40
45
50
55
60
65

1
5
10
15
20
25
30
35
40
45
50
55
60
65

1
5
10
15
20
25
30
35
40
45
50
55
60
65

f g h i j

1
5
10
15
20
25
30
35
40
45
50
55
60
65

f g h i j


1
5
10
15
20
25
30
35
40
45
50
55
60
65

1
5
10
15
20
25
30
35
40
45
50
55
60
65

Sample Lab Reports

- I did 2/5 of Lab 1; Jose did 4/5.
 - I would have given my own report (if 5/5 done) an A-
 - Jose would have given his own report (if 5/5 done) an A-
- <http://positron.hep.upenn.edu/pet/wiki/index.php/Us>
- <http://positron.hep.upenn.edu/pet/wiki/index.php/Us>
- Note that Jose will be grading the reports

Series and parallel resistors, mesh currents, node voltages, Thevenin and Norton. (a) Write down the equations for the mesh currents I_{1-4} in figure 2.25, but do not solve them. (b) Find the current $I_3 + I_4$ supplied by the battery by simplifying series and parallel combinations of resistors. (c) Find V_1 and V_2 . (d) Hence find I_{1-4} and check them against (a). (e) Find the Thevenin equivalent of the circuit to the left of AB ; use this to check I_4 . (f) Find the Norton equivalent of the circuit across the terminals CD . Use this to check $I_3 + I_4$. (g) Find the Norton equivalent of the circuit to the right of EF ; use it to check I_1 . (Ans: (a) $I_3 + I_4 = 2$ A; (c) $V_1 = 8$ V; $V_2 = 8/3$ V; (d) $I_1 = 1/9$ A; $I_2 = 2/9$ A; $I_3 = 2/3$ A; $I_4 = 4/3$ A; (e) $V_{EQ} = 144/14$ V, $R_{EQ} = 24/14$ Ω ; (f) $I_{EQ} = 3$ A, $R_{EQ} = 4$ Ω ; (g) $I_{EQ} = 18/19$ A, $R_{EQ} = 24 \times 19/143$ Ω .)

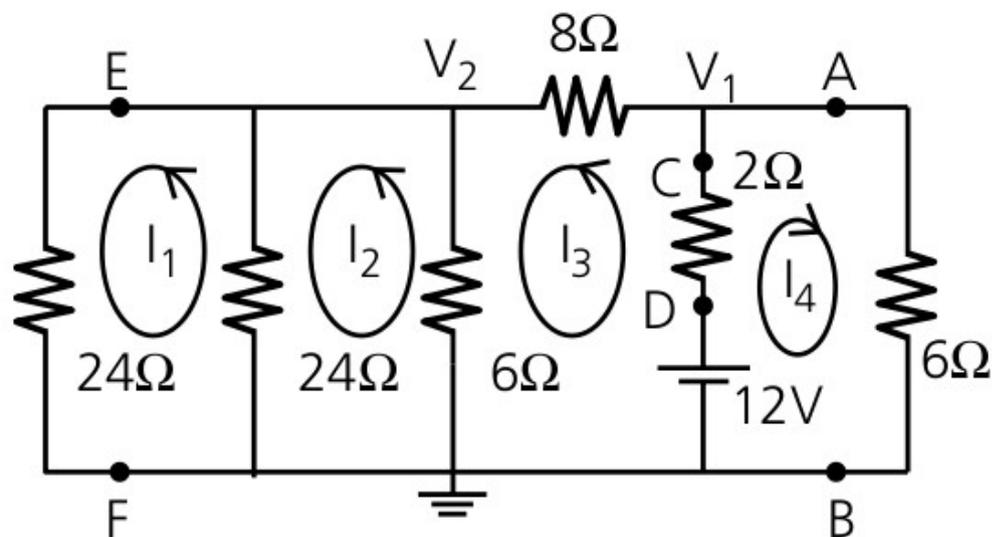

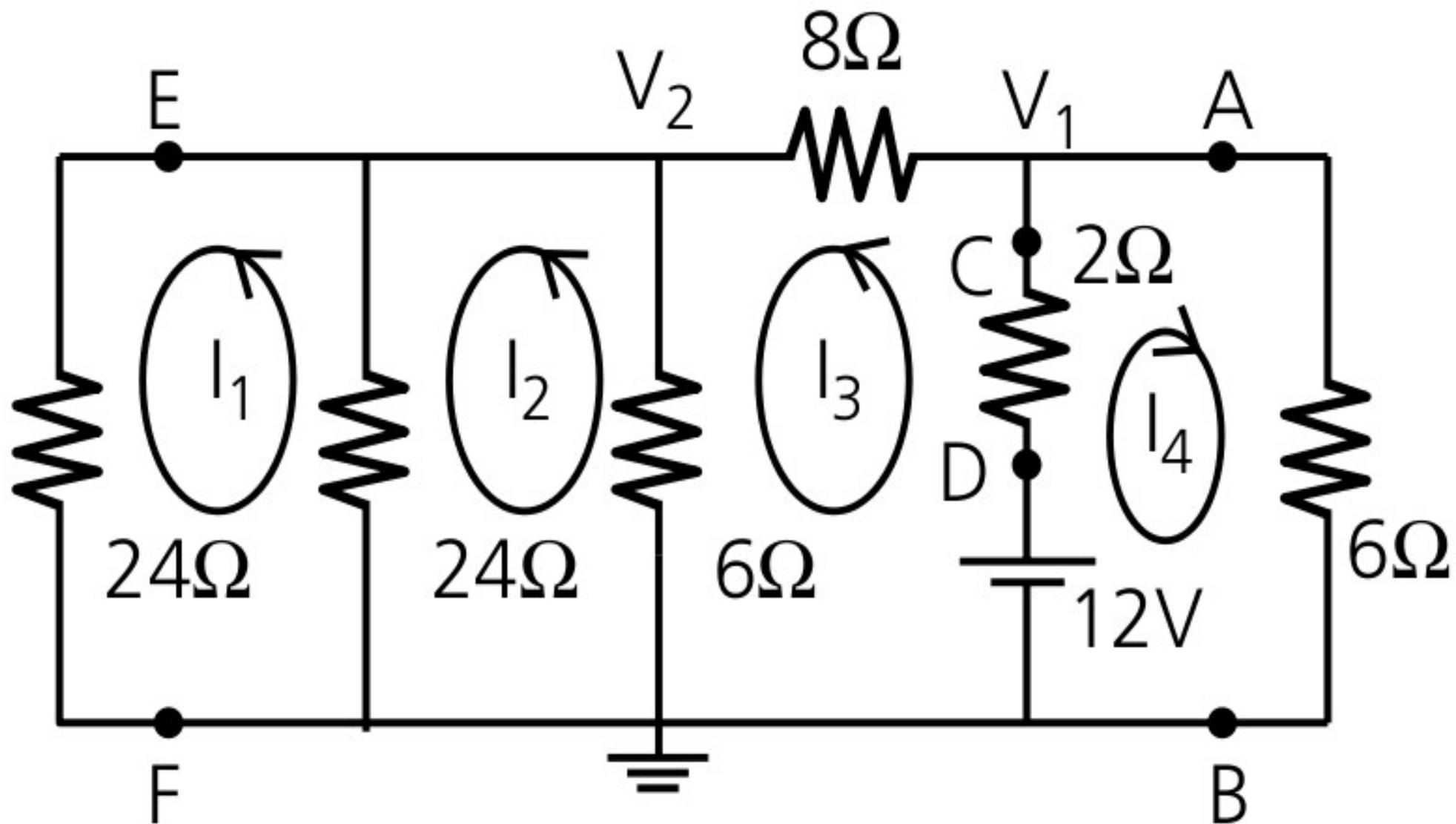


Fig. 2.25.

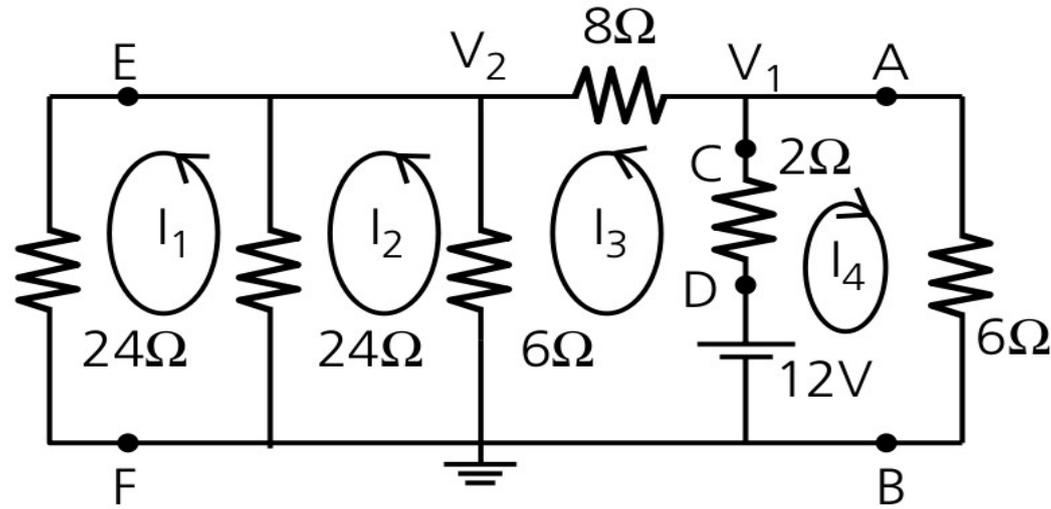


Fig. 2.25.

Series and parallel resistors, mesh currents, node voltages, Thevenin and Norton. (a) Write down the equations for the mesh currents I_{1-4} in figure 2.25, but do not solve them. (b) Find the current $I_3 + I_4$ supplied by the battery by simplifying series and parallel combinations of resistors. (c) Find V_1 and V_2 . (d) Hence find I_{1-4} and check them against (a). (e) Find the Thevenin equivalent of the circuit to the left of AB ; use this to check I_4 . (f) Find the Norton equivalent of the circuit across the terminals CD . Use this to check $I_3 + I_4$. (g) Find the Norton equivalent of the circuit to the right of EF ; use it to check I_1 .