

①

PHYSICS 364, 2010-10-18

Bill
ASHMANSKAS

We'll cover a few more bipolar-junction transistor circuits today, mostly linear / amplifier-related.

Next week we'll introduce FETs, and we'll focus on transistor circuits that basically work as switches — ON or OFF — vs. linear behavior.

For next week, read either HH ch. 3 or Bugg FET material in ch 10, §17.7, §18.11. We'll do a quiz that covers only material through this week (BJTs).

One note from last Thursday:

$$\frac{dI_c}{dV_{BE}} = \frac{I_c}{25\text{mV}} \Rightarrow \frac{dV_{BE}}{d(\log_{10}(I_c))} = 2.3 \times 25\text{mV} \approx \boxed{\frac{60\text{mV}}{\text{decade}}}$$

(at room temperature)

(on the lab board, I had forgotten that $\log(10) \approx 2.3$!)

BJT circuits today


current source
switch
current mirror
differential amplifier
simple opamp

Lab #5 is now due
on 10-25 (merge w/ #6)

Optional parts are now
required.

I will write up differential
amplifier, etc., as add-ons
to Lab #5/6.

② BJT current source

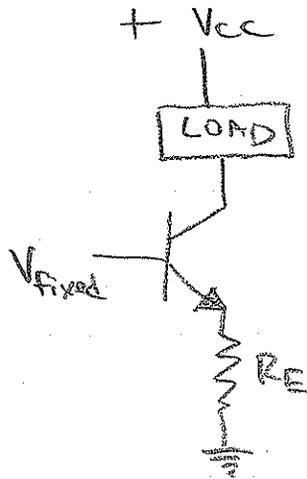

$$I_C \approx I_E = \frac{V_{\text{fixed}} - V_{BE}}{R_E}$$


Notes:

- only works as long as V_{CE} stays out of saturation region.

- $\frac{dV_{CE}}{dI_C} = \text{source impedance}$


r_s is large but not infinite.

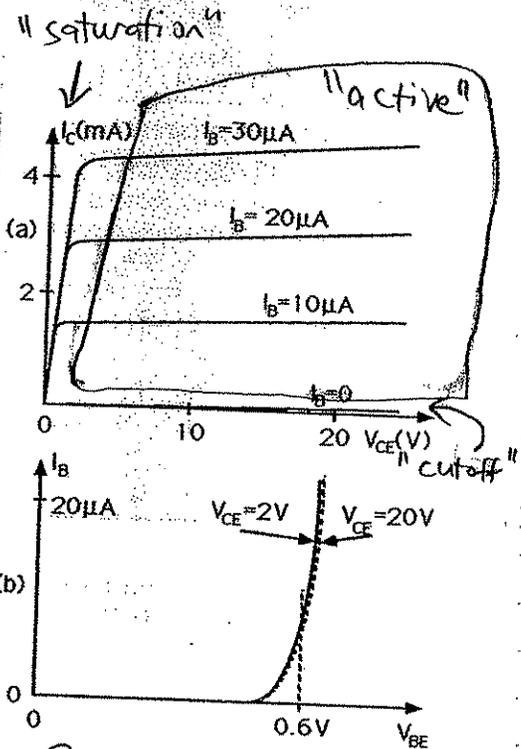(Ideal current source has $R_{out} = \infty$.)




Bugg.
Fig. 9.30. Characteristics of the bipolar transistor.

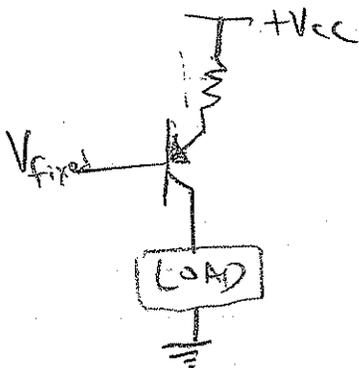Can use PNP for true current source (vs. current "sink" shown above):




3

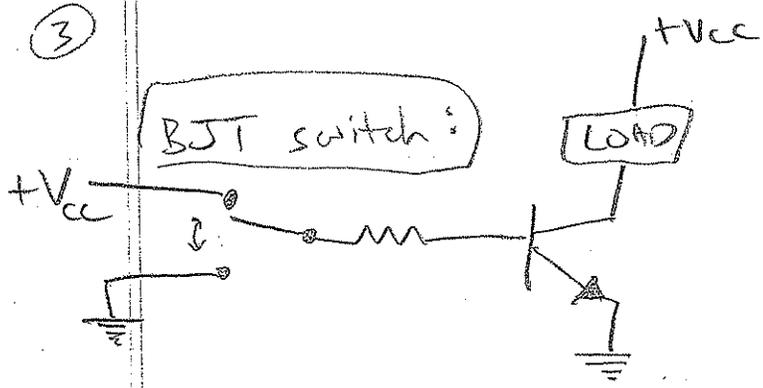


drive base either down to cutoff or up to saturation.

(much more on transistor switches next week)

current mirror

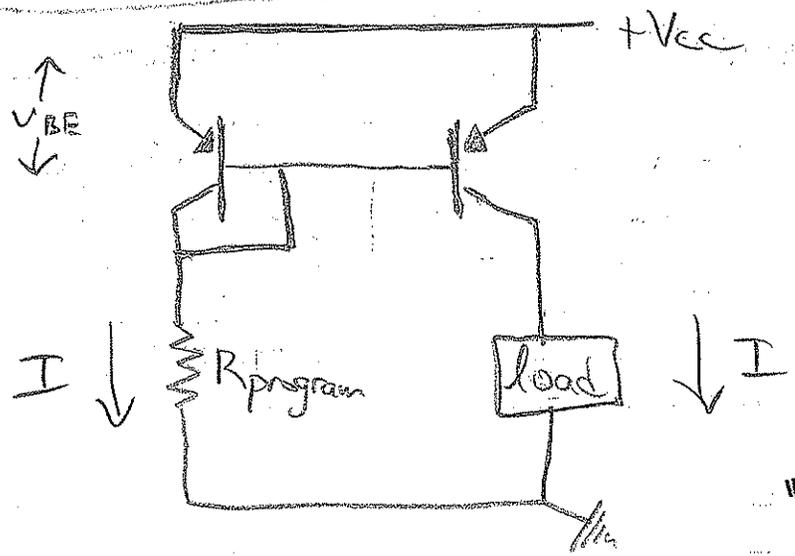

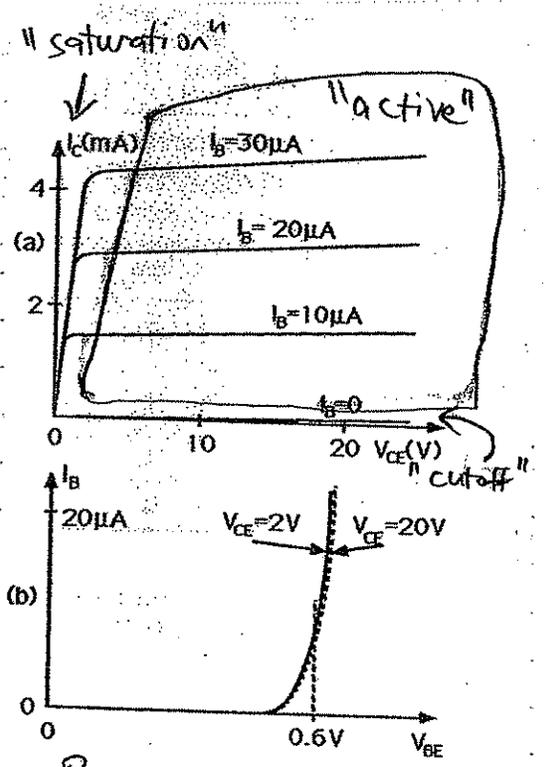
Again, finite (though very large) impedance because I_c vs. V_{CE} is not quite flat ("Early effect")



BUGG.
Fig 9.30. Characteristics of the bipolar transistor.

④

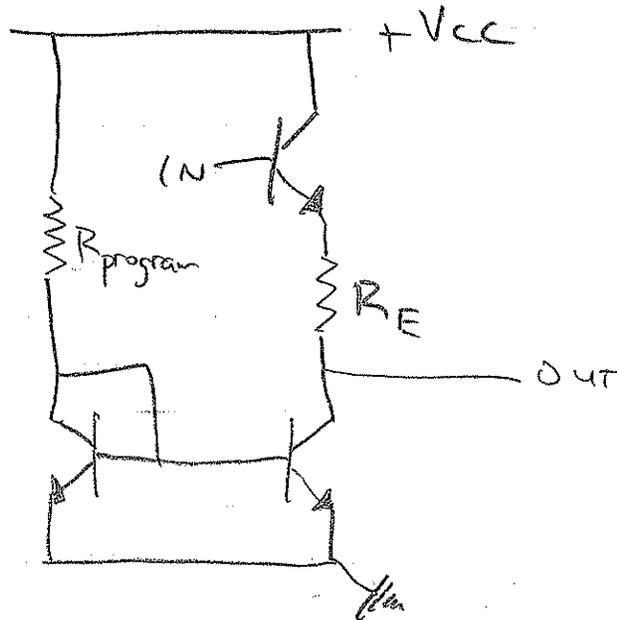Cute current mirror application (from Bugg's book): level shifter



$$I = \frac{V_{cc} - V_{BE}}{R_{program}}$$

$$V_{out} = V_{in} - V_{BE} - I \cdot R_E$$

DIGRESSION: corny emitter follower mnemonic from Hayes & Horowitz

Hayes & Horowitz

And here is a corny mnemonic device to describe this impedance-changing effect. Imagine an ill-matched couple gazing at each other in a dimly-lit cocktail lounge—and gazing through a rose-colored lens that happens to be a follower. Each sees what he or she wants to see:


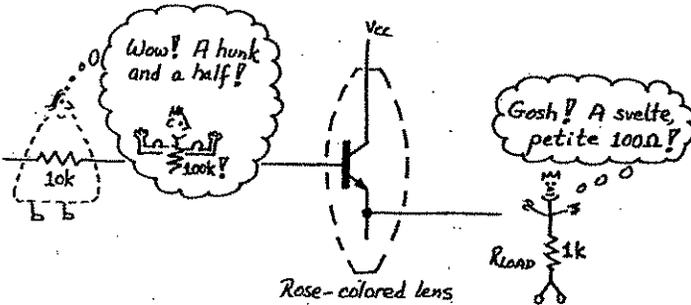


Figure N4.4: Follower as rose-colored lens: it shows what one would like to see

5

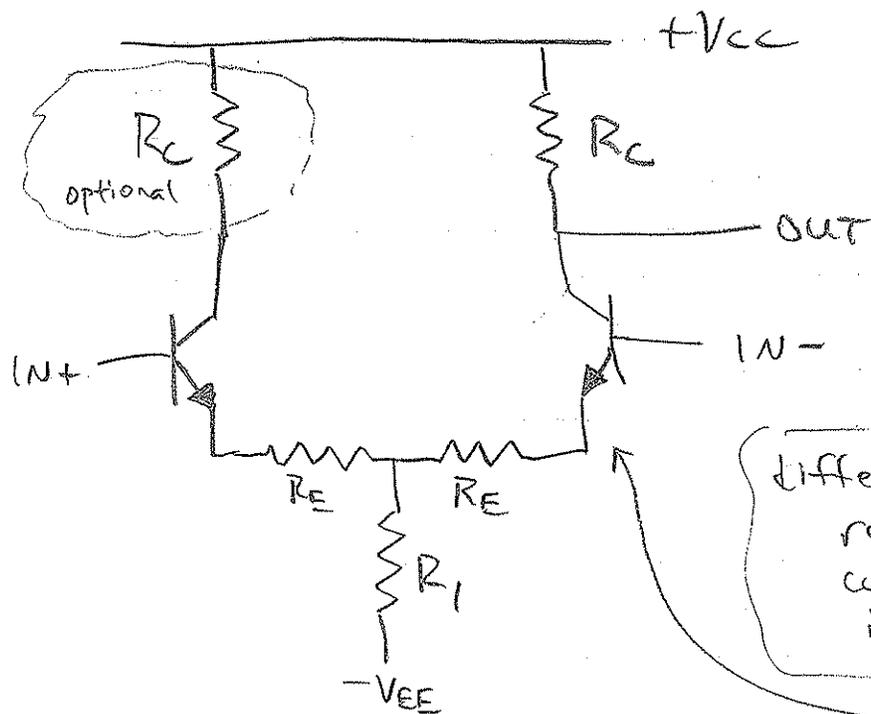Differential amplifier ("long-tailed pair")



Differential signal: $v \equiv \Delta V_+ - \Delta V_-$
 $\Delta V_{IN+} = v/2, \Delta V_{IN-} = -v/2$

include "re" from transistor

$$\Delta I_C^- = \Delta V^- / R_E \Rightarrow \Delta V_{OUT} = - \frac{\Delta V^- \cdot R_C}{R_E + r_e} = \frac{v R_C}{2(R_E + r_e)}$$

Common-mode signal: $v \equiv \Delta V^+ = \Delta V^-$

$$\Delta I_C^+ = \Delta I_C^- = \frac{v}{(R_E + r_e + 2R_1)} \Rightarrow \frac{V_{OUT}}{V_{CM}} = - \frac{R_C}{2R_1 + R_E + r_e}$$



$$CMRR = \frac{2R_1 + R_E + r_e}{2(R_E + r_e)} \rightarrow \frac{R_1}{R_E + r_e} \text{ for } R_1 \gg R_E$$

(recall $r_e = \frac{25mV}{I_C}$ from diode curve slope)

- Best CMRR \Rightarrow remove R_E and replace R_1 with current source
- Highest gain \Rightarrow replace R_C with current mirror

6

Differential amp examples

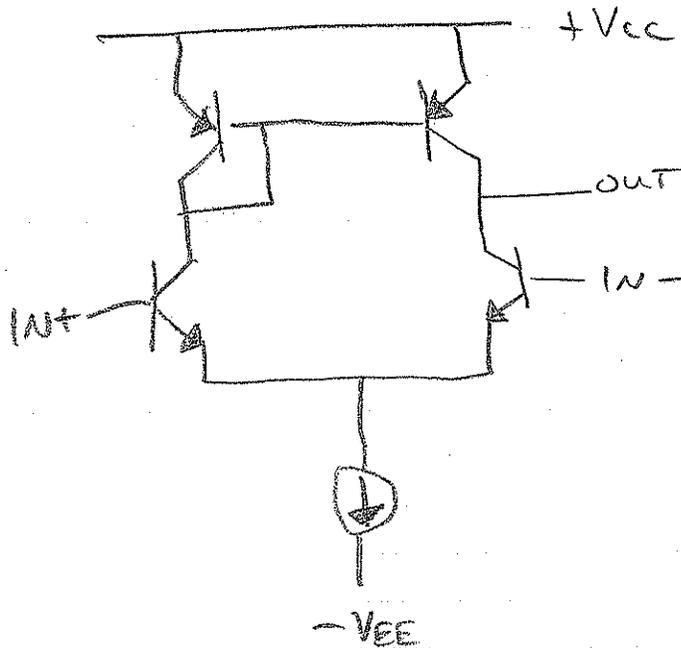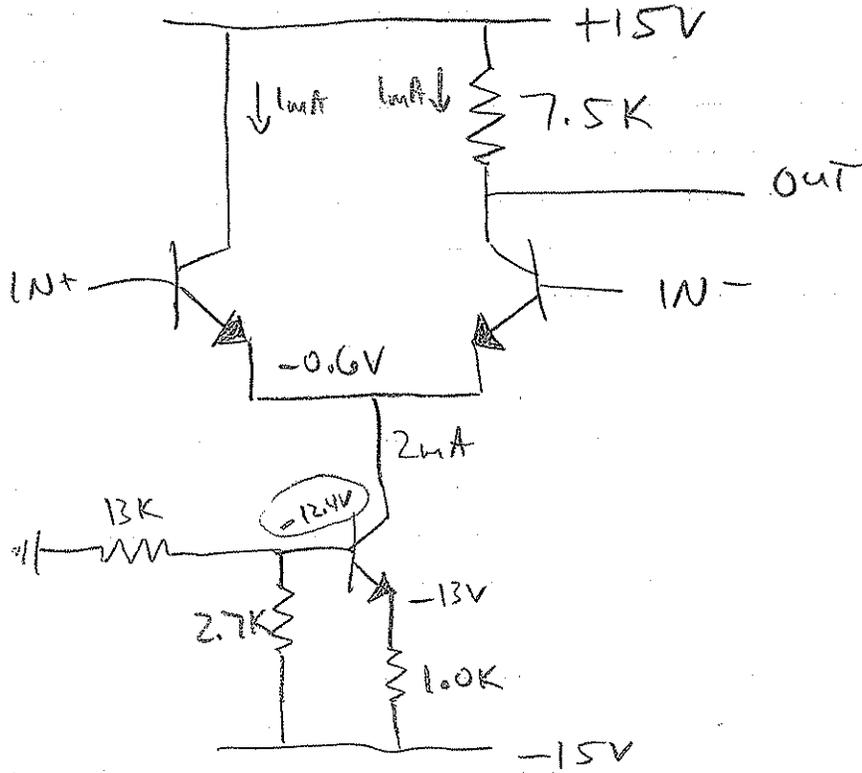


Note: can ground IN- on diff. amp to get single-ended DC amplifier.

⇒ no annoying diode drops; temperature compensation

7

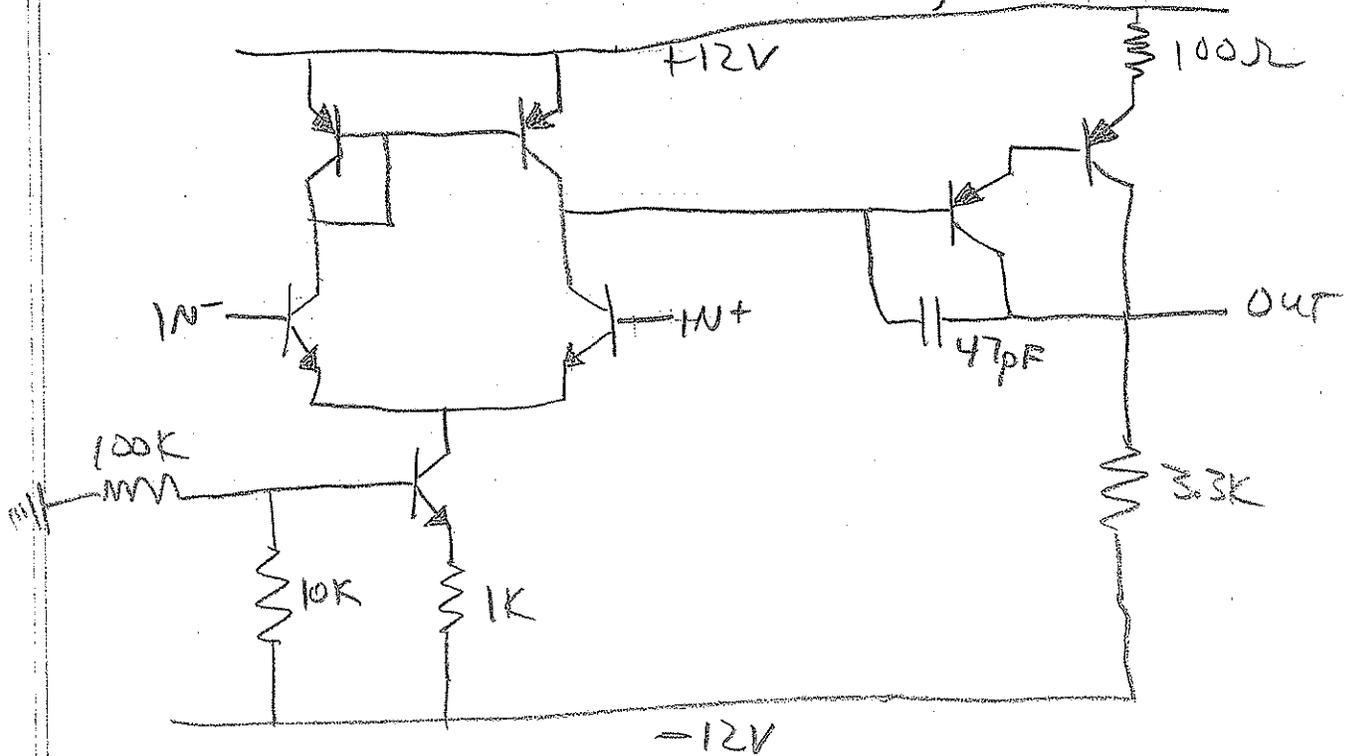I found this relatively simple opamp circuit on web (EE 332, R.B. Darling, Washington.edu)



Note Darlington $\Rightarrow \beta^2$

Note compensation capacitor

\Rightarrow "Miller effect"

capacitance multiplied
by voltage gain


⑧ Simplify circuit a bit:

remove current source from tail ;

remove Darlington

reduce bandwidth

⇒ works OK in SPICE, as an opamp.

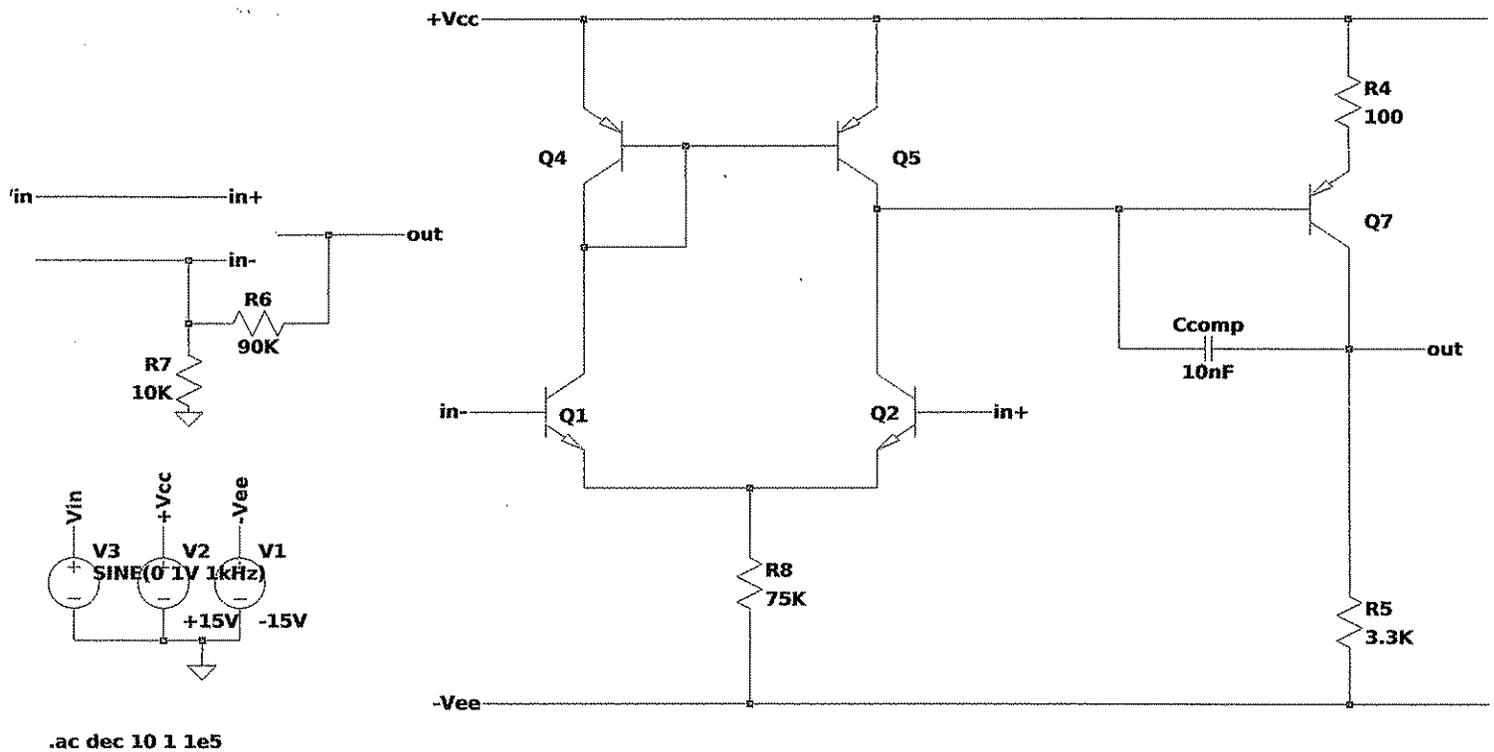

DIGRESSION: corny emitter follower mnemonic from Hayes & Horowitz

Hayes & Horowitz

And here is a corny mnemonic device to describe this impedance-changing effect. Imagine an ill-matched couple gazing at each other in a dimly-lit cocktail lounge—and gazing through a rose-colored lens that happens to be a follower. Each sees what he or she wants to see:


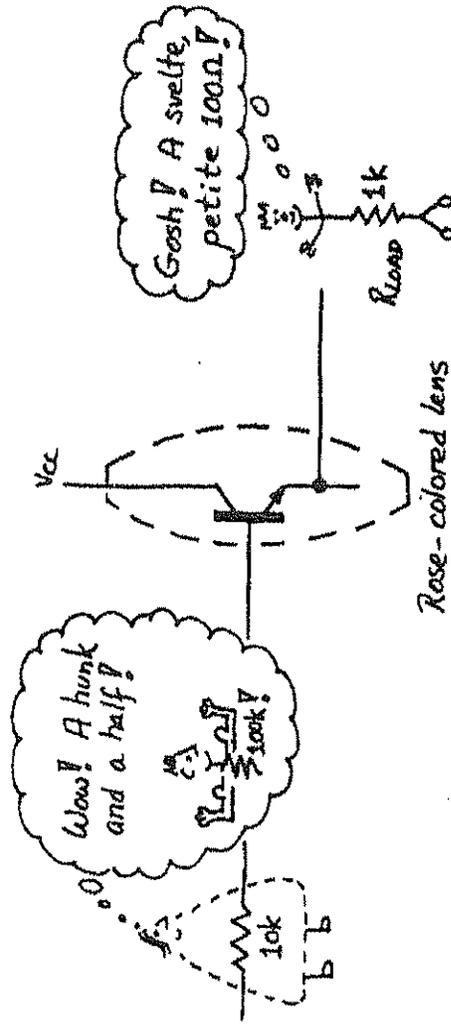


Figure N4.4: Follower as rose-colored lens: it shows what one would like to see

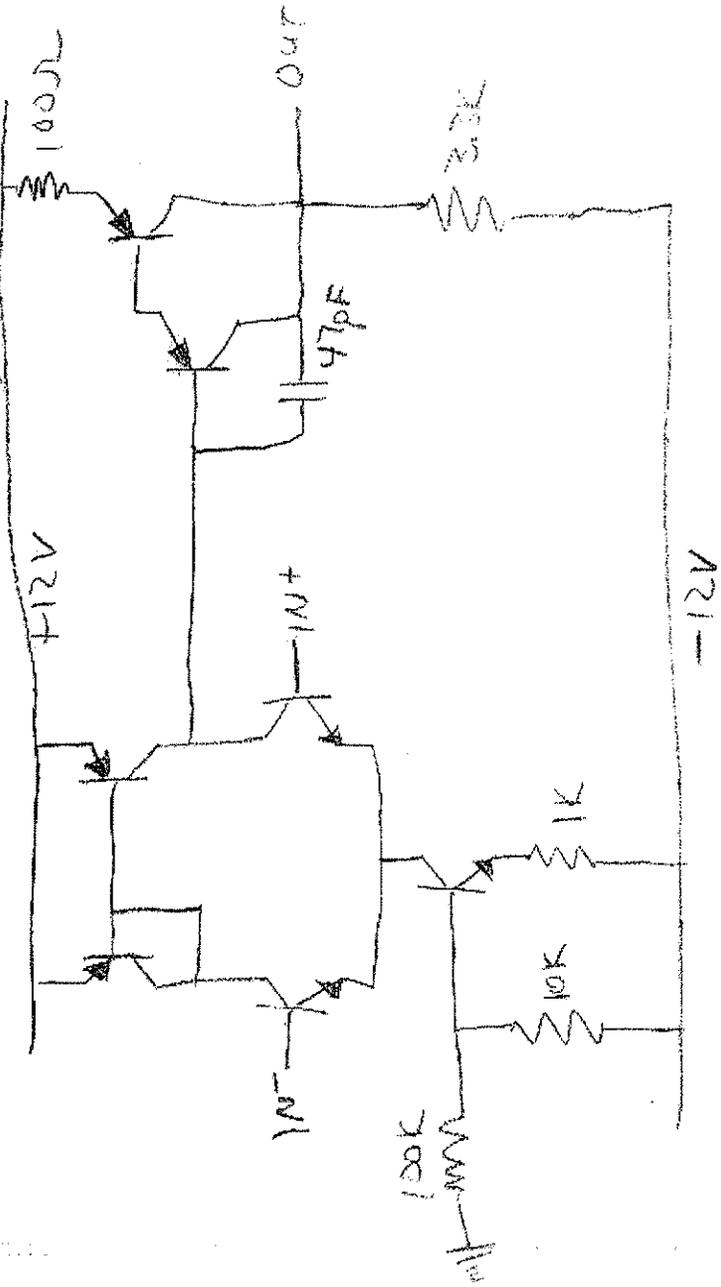I found this relatively simple opamp circuit on web (EE 332 R.B. Darling, Washington.edu)



Note Darlington $\Rightarrow \beta^2$

Note compensation capacitor

\Rightarrow " Miller effect "

capacitance multiplied by voltage gain


Simplify circuit a bit:


Remove current source from tail;




Remove Darlington

Reduce bandwidth



⇒ works OK in SPICE, as a sump.

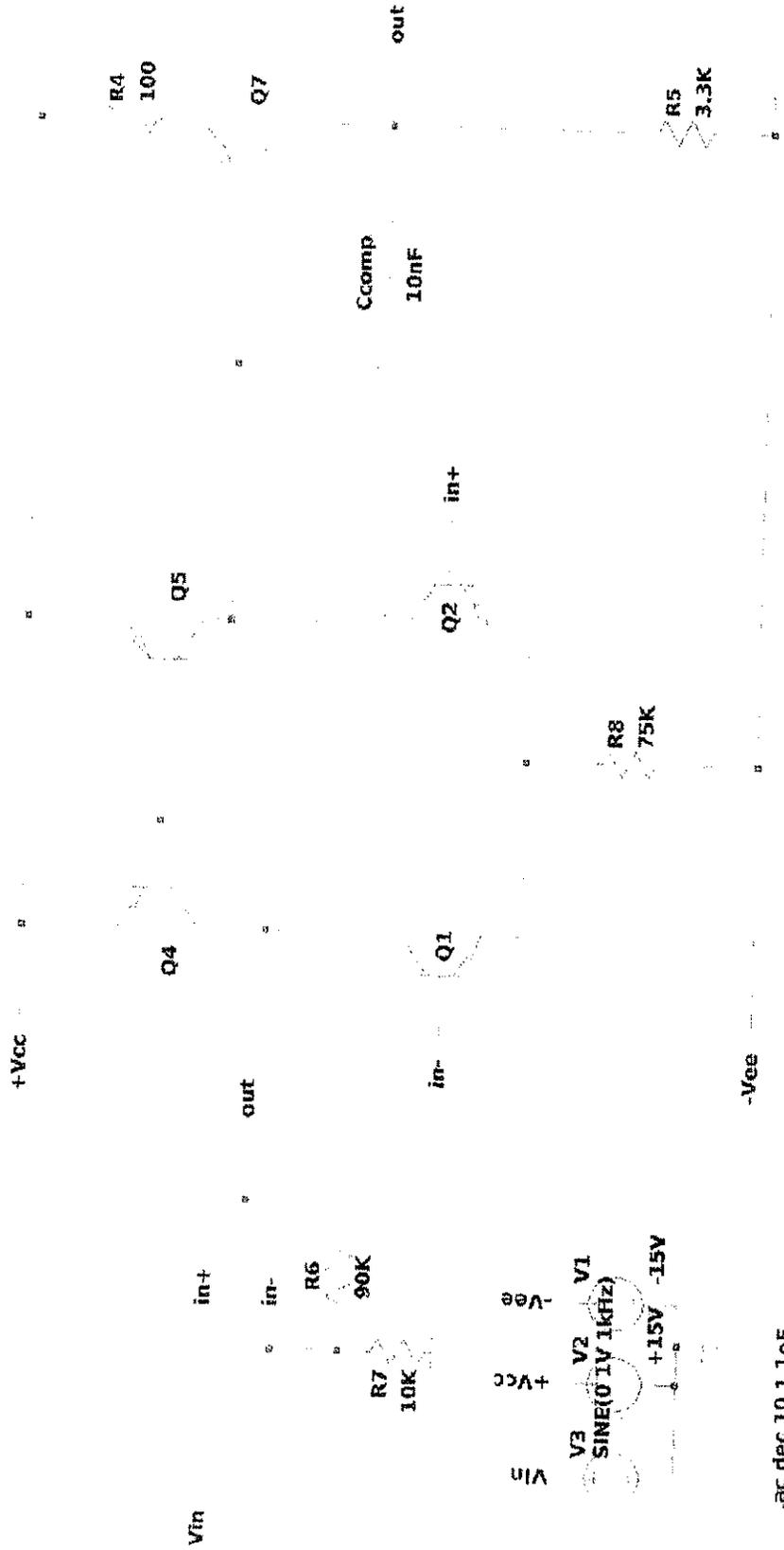


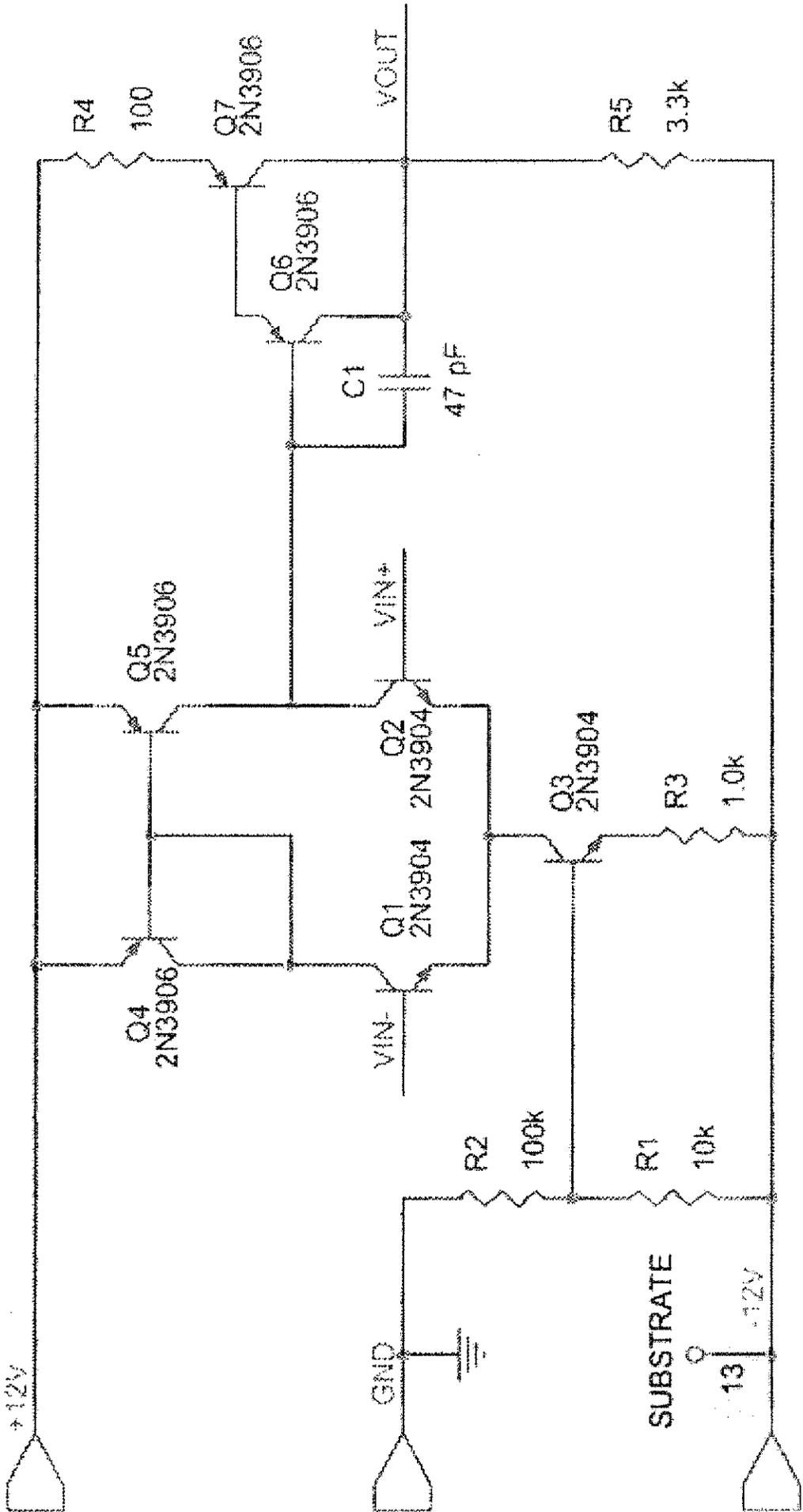


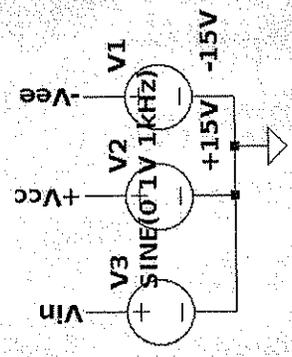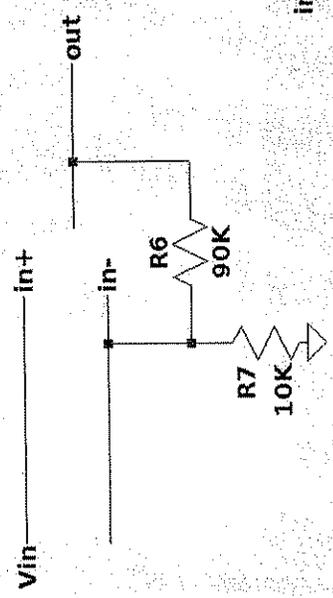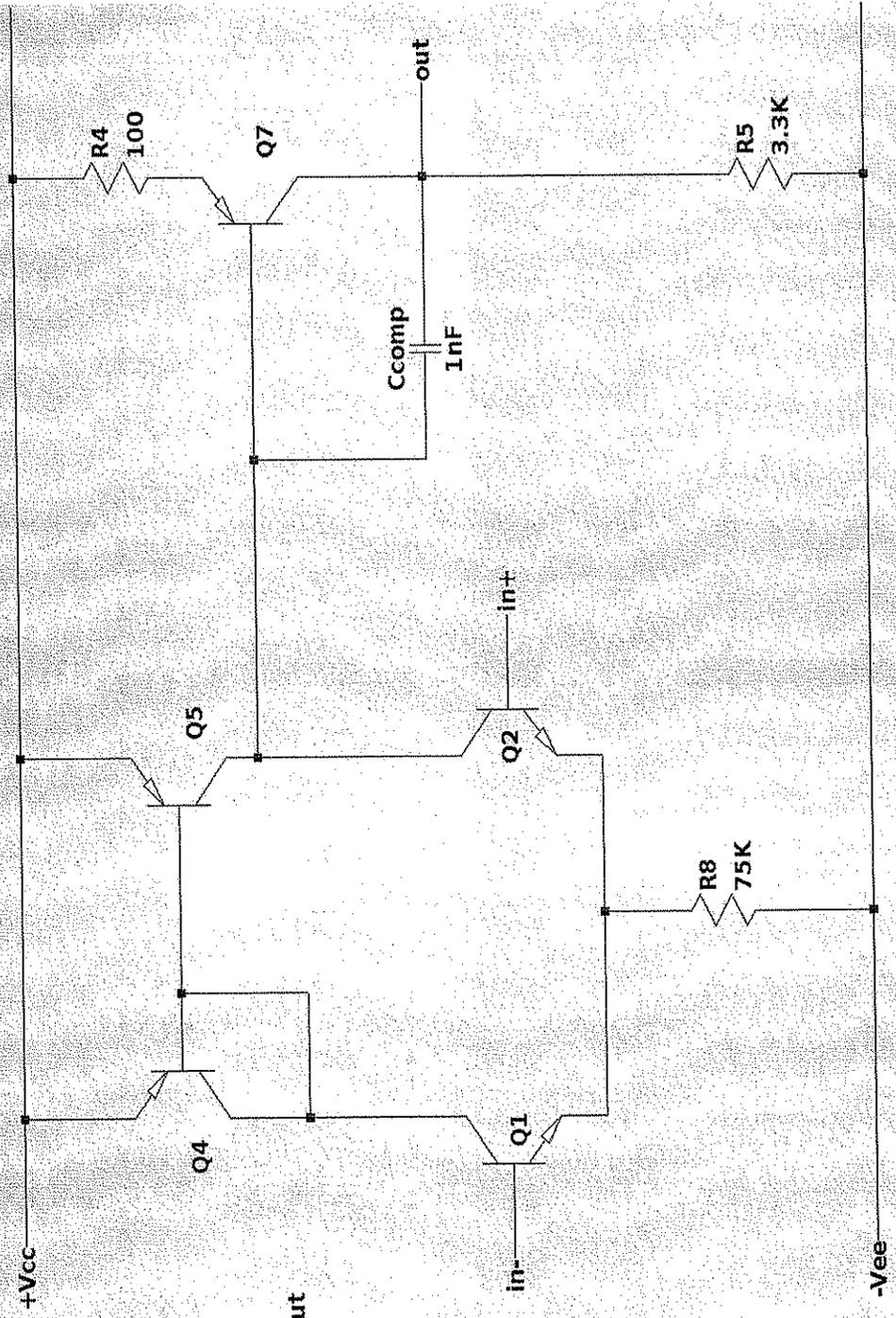

.ac dec 10 1 1e6

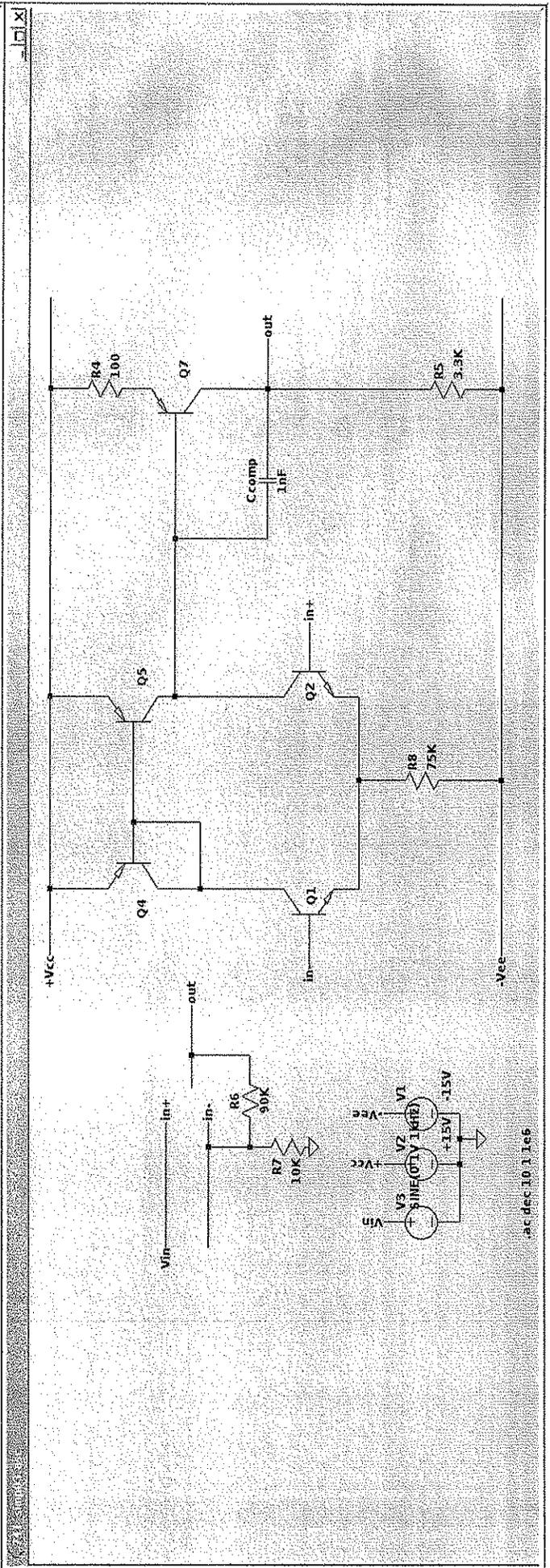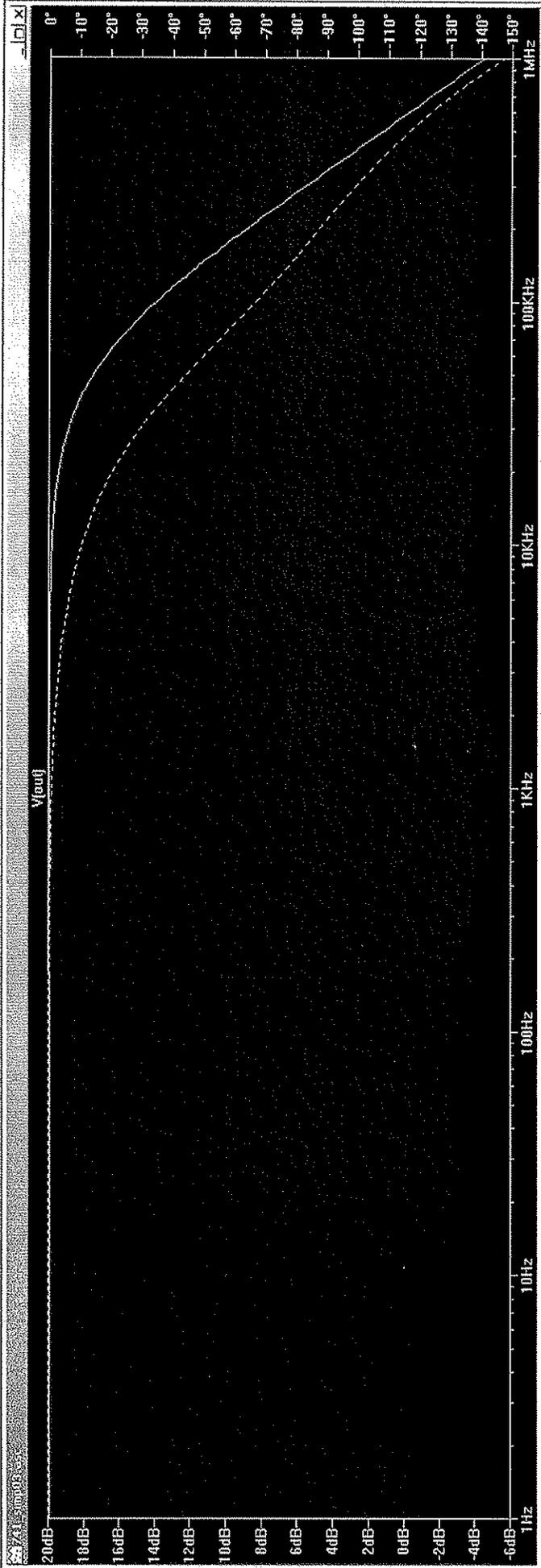

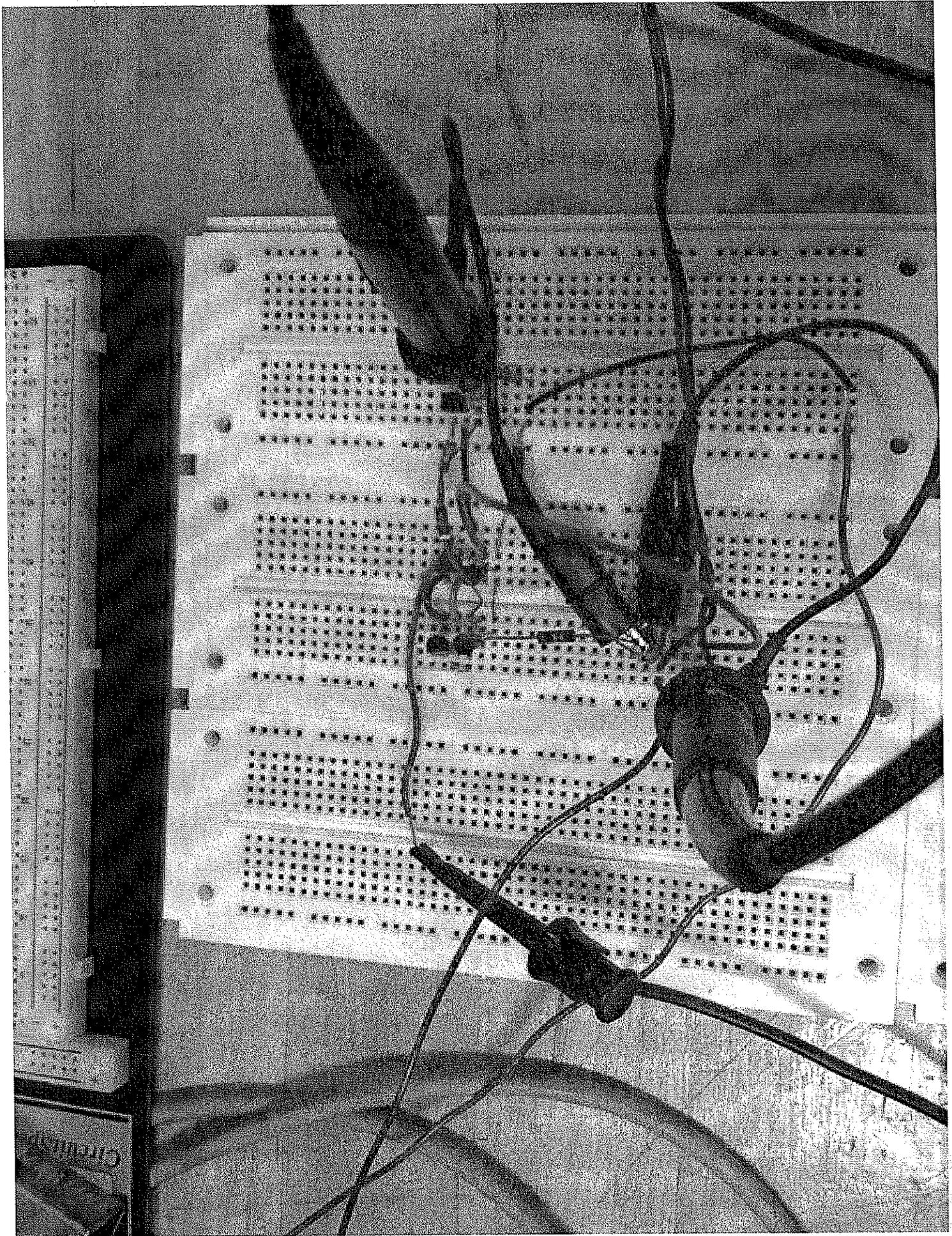

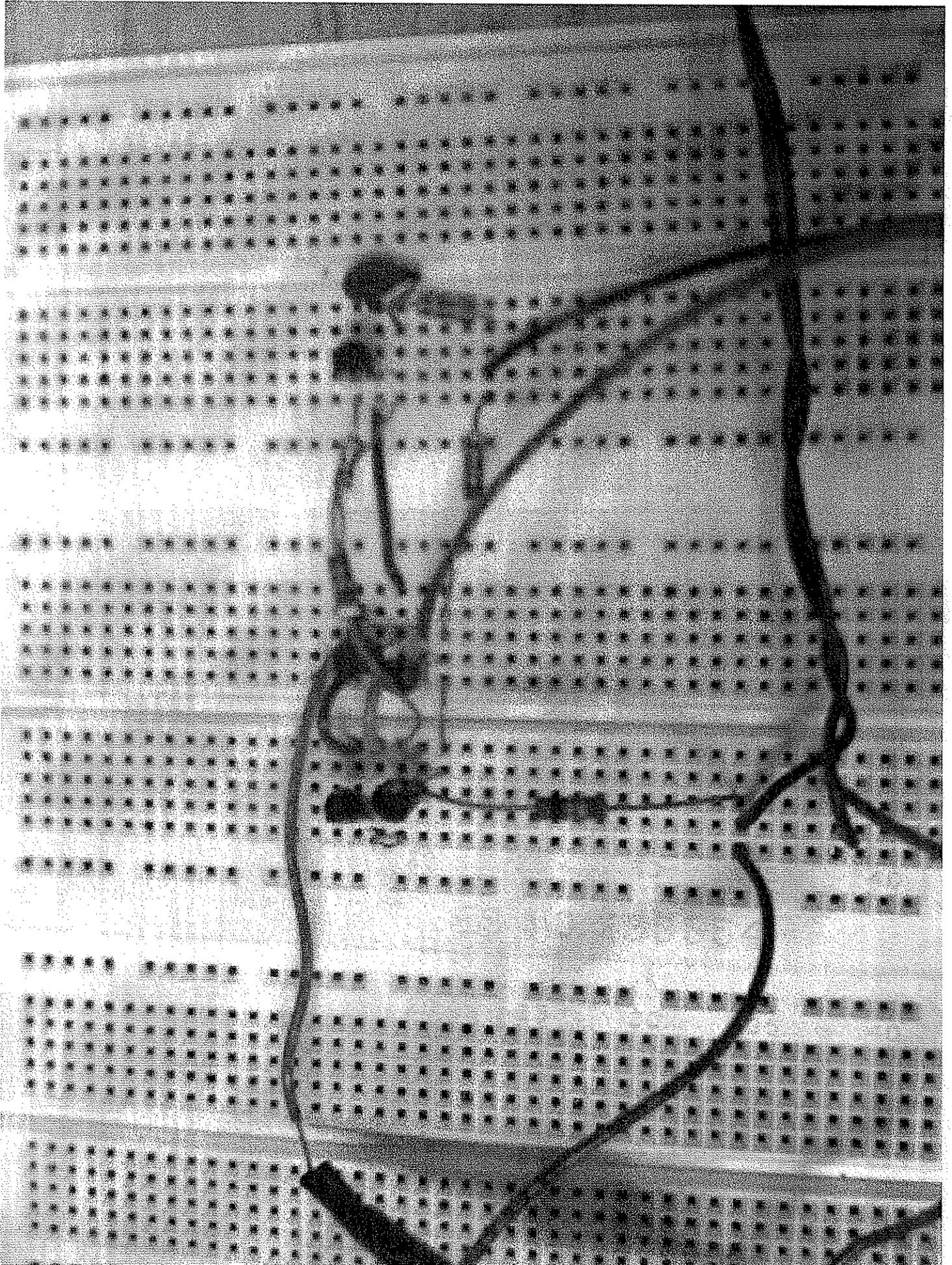


10k

1k

100V

100ms

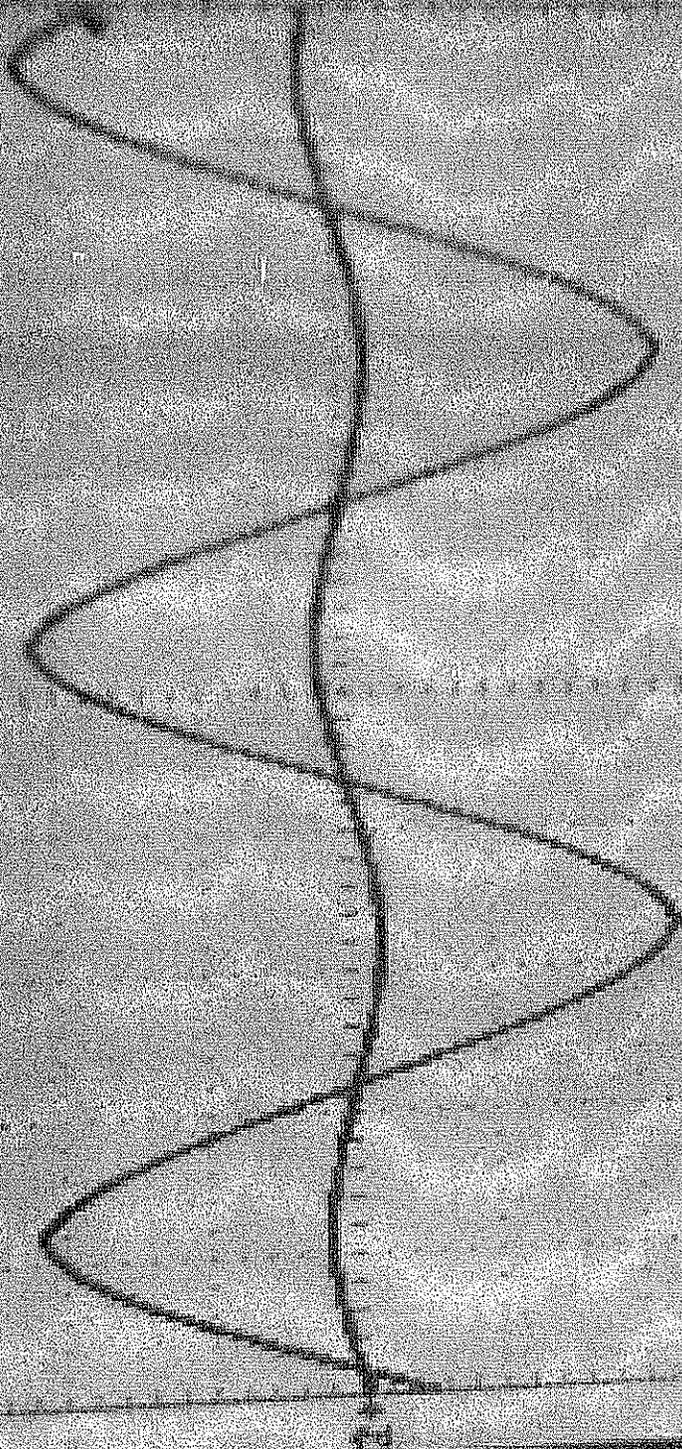


CH1 1.00V

CH2 1.00V

100.1ms

100ms

CH1 1.00V

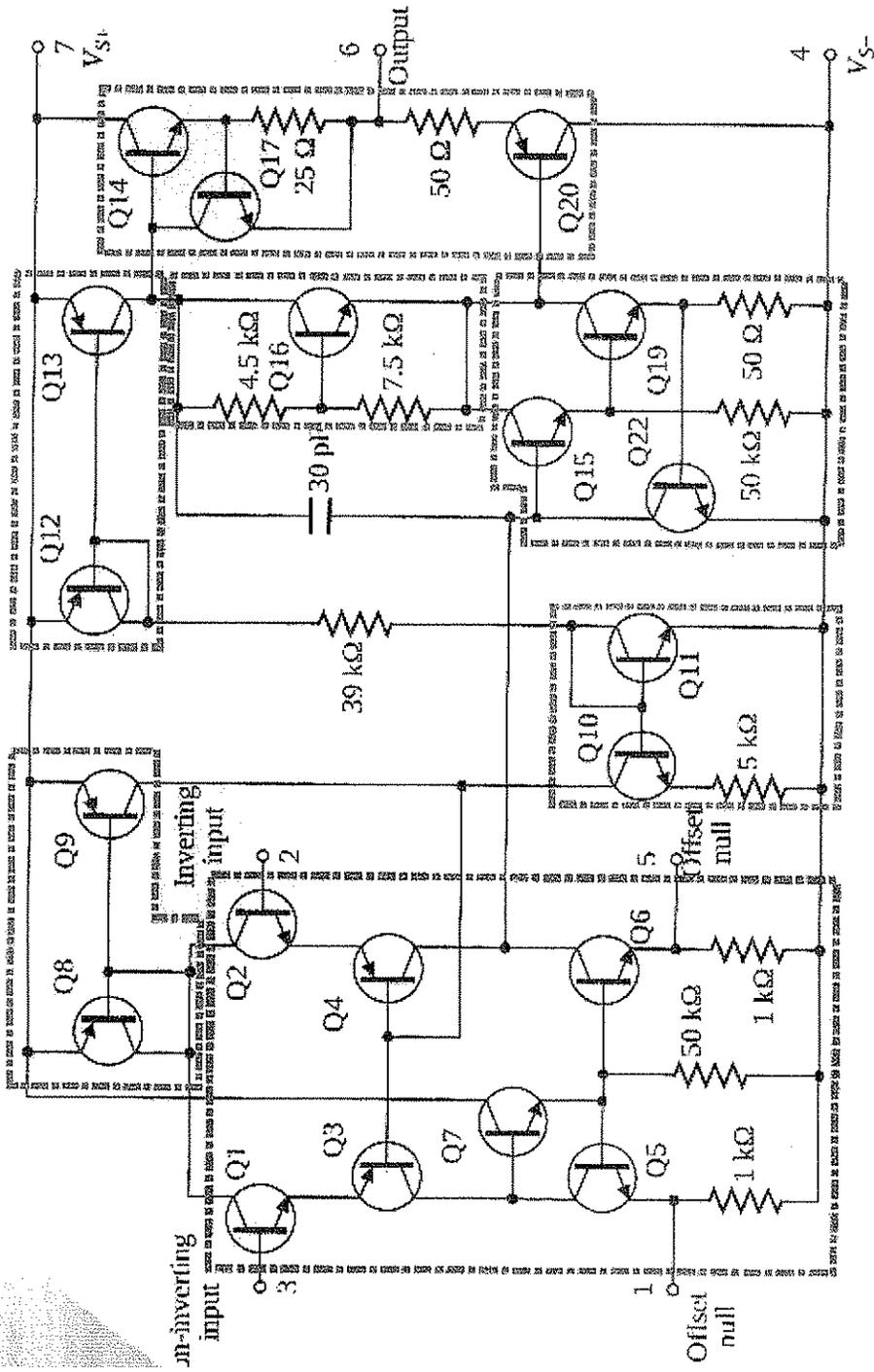

You should now recognize
 more pieces of the
 741 schematic. (In this
 case, I'm using Wikipedia
 "opamp" entry.)